

Current, Voltage, Power & Resistance with Resistors in Parallel Circuits (Lab 7)

Incorporating all Electrical Elements

Leonardo Fusser, 1946995

Experiment Performed on **16 October 2019**
Report Submitted on **21 October 2019**

Department of Computer Engineering Technology
Circuit Analysis & Simulation I
Mohamed Tavakoli

VANIER
C É G E P / C O L L E G E
Learning today Leading tomorrow

TABLE OF CONTENTS

1.0 Purpose.....	3
2.0 Equipment Needed.....	3
3.0 Theory.....	3
4.0 Experiemntal Results	4
5.0 Conclusion	6

1.0 PURPOSE

- Measuring wattage (power) across resistors.
- Measuring resistance across resistors.
- Measuring voltage across resistors.
- Measuring current through resistors.

2.0 EQUIPMENT NEEDED


- (1x) desktop Power Supply.
- (1x) desktop Digital Multimeter.
- (3x) 4-band (1/4 watt) resistors.
- (1x) electronics breadboard.

3.0 THEORY

Calculating Power, Resistance, Current & Voltage in Parallel Circuits

- A **PARALLEL** circuit consists of having two elements sharing two points in common (refer to Document #1).

(Document #1 – Parallel Circuits)

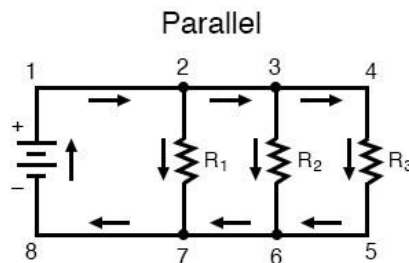

Formula to calculate total RESISTANCE in ohms (Ω):

$$\frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_{N...}}$$

Formula to calculate source current in Amperes (A):

$$I_s = \frac{E}{R_{EQ}}$$

Formula to calculate the current through the elements in Amperes (A):

$$I_s = I_1 + I_2 + I_3 + I_{N...}$$

Formula to calculate the voltage across each resistor in Volts (V):

$$E = V_1 = V_2 = V_3 = V_{N...}$$

Formula to calculate power dissipated by each element in Watts (W):

$$[P_1 = V_1 I_1] [P_2 = V_2 I_2] [P_3 = V_3 I_3] [P_N = V_N I_{N...}]$$

Formula to calculate power delivered by the source in Watts (W):

$$P_{del} = EI$$


Formula to calculate the total power dissipated by the elements in Watts (W):

$$P_{del} = P_1 + P_2 + P_3 + P_{N...}$$

4.0 EXPERIMENTAL RESULTS

Results from the Procedure section:

Fig.2

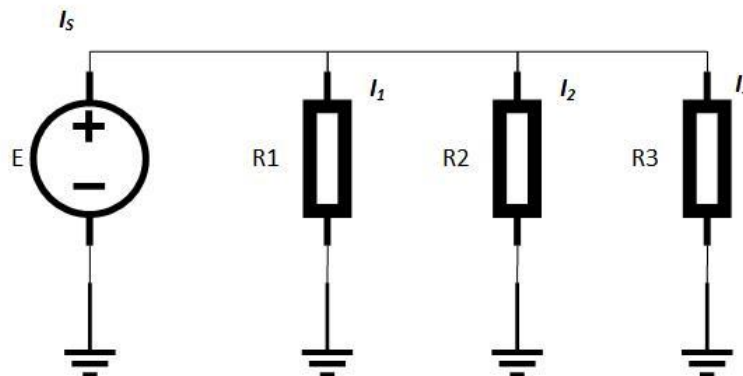

PROCEDURE:

- Step 1: Calculate by color code and Measure the values of the resistors, and copy to Table 1.
- Step 2: Calculate voltages of each resistor and copy to Table 1.
- Step 3: Calculate the power dissipated in each resistor and write in Table 1.
- Step 4: Calculate the current in each resistor and write in Table 1.
- Step 5: Build the circuit of Fig.2.
- Step 6: Ask your teacher to verify your circuit before you connect power supply.
- Step 7: Set the voltage source to 12V and limit the current to 500mA.
- Step 8: Measure the current of each resistor and copy to Table 1.
- Step 9: Verify the equations (2), (3), (4) and (5).

Table 1		Voltage of Resistors			Current			
Resistor	Value	Calculated	Measured	%Error	Calculated	Measured	%Error	Power
R1	1KΩ	12V	11.99V	0.08%	12mA	12.10mA	0.8%	144mW
R2	2.2KΩ	12V	11.99V	0.08%	5.45mA	5.40mA	0.9%	65.4mW
R3	3.2KΩ	12V	11.99V	0.08%	3.75mA	3.60mA	4%	45mW

CALCULATIONS:

(%Error Voltage of Resistors)

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{11.99V - 12V}{12V} * 100 = 0.08\% \text{ (Same for the others below in the table)}$$

(Calculated Current)

$$V = I * R, 12 = I * 1K\Omega, I = 12mA$$

$$V = I * R, 12 = I * 2.2K\Omega, I = 5.45mA$$

$$V = I * R, 12 = I * 3.2K\Omega, I = 3.75mA$$

(%Error Current)

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{12.10mA - 12mA}{12mA} * 100 = 0.8\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{5.40mA - 5.45mA}{5.45mA} * 100 = 0.9\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{3.60mA - 3.75mA}{3.75mA} * 100 = 4\%$$

(Power)

$$P = I * V, P = 12mA * 12V, P = 144mW$$

$$P = I * V, P = 5.45mA * 12V, P = 65.4mW$$

$$P = I * V, P = 3.75mA * 12V, P = 45mW$$

5.0 CONCLUSION

- Purpose of this lab has been achieved.
- Understood how to measure power across the 3 resistors and voltage source.
- Understood how to measure resistance across the 3 resistors in the circuit.
- Understood how to measure voltage across the 3 resistors in the circuit.
- Understood how to measure current through the 3 resistors in the circuit.
- Adapted/ learned more advanced functions in lab equipment (PLCs, store function, etc...)