

# **Computational Logic Circuits (Online Lab 2)**

## *Synchronous Counters*

**Leonardo Fusser, 1946995**

Experiment Performed on **17 April 2020**  
Report Submitted on **22 April 2020**

**Department of Computer Engineering Technology**  
*Computational Logic Circuits*  
*Subash Handa*

## **TABLE OF CONTENTS**

|                   |   |
|-------------------|---|
| Objectives .....  | 3 |
| Design .....      | 3 |
| Simulations ..... | 3 |
| Questions.....    | 6 |

## OBJECTIVES

- To understand the function and application of synchronous counters.
- To understand how to design a synchronous counter.
- To verify and simulate the function of a 3-bit synchronous counter.

## DESIGN

### Experiment


- There was one simulation done in this lab. First, we were asked to do general research on synchronous counters. Following the research, we were asked to design a 3-bit synchronous counter that goes through a certain sequence. The simulations were done in "Logisim". Below outlines the work done in the lab.

## SIMULATIONS

### Simulations from the Experiment

Simulation made by: Leonardo Fusser (1946995)

For: Subash Handa  
Computational Logic  
Online Lab #2, Simulation 1

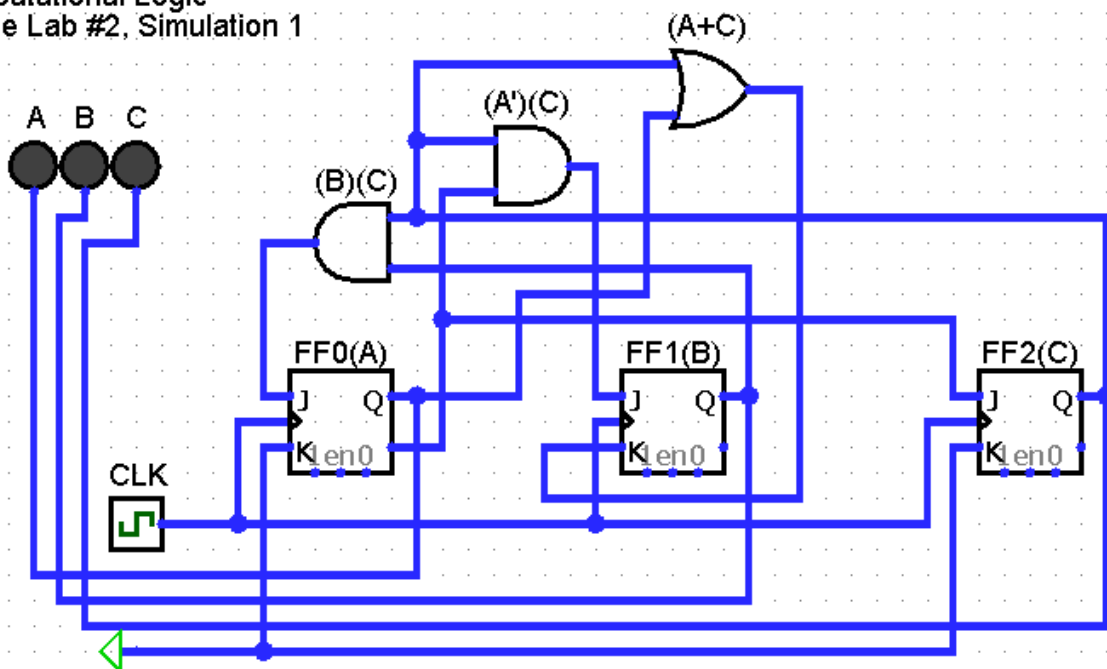

Custom 3-bit synchronous counter simulation (above)

Custom 3-bit synchronous counter truth table

| State | (PRESENT) |       |       | (NEXT)    |           |           | J-K Flip Flops |       |       |
|-------|-----------|-------|-------|-----------|-----------|-----------|----------------|-------|-------|
|       | $A_N$     | $B_N$ | $C_N$ | $A_{N+1}$ | $B_{N+1}$ | $C_{N+1}$ | JA/KA          | JB/KB | JC/KC |
| 0     | 0         | 0     | 0     | 0         | 0         | 1         | 0 X            | 0 X   | 1 X   |
| 1     | 0         | 0     | 1     | 0         | 1         | 0         | 0 X            | 1 X   | X 1   |
| 2     | 0         | 1     | 0     | 0         | 1         | 1         | 0 X            | X 0   | 1 X   |
| 3     | 0         | 1     | 1     | 1         | 0         | 0         | 1 X            | X 1   | X 1   |
| 4     | 1         | 0     | 0     | 0         | 0         | 0         | X 1            | 0 X   | 0 X   |
| 5     | 1         | 0     | 1     | 0         | 0         | 0         | X 1            | 0 X   | X 1   |
| 6     | 1         | 1     | 0     | 0         | 0         | 0         | X 1            | X 1   | 0 X   |
| 7     | 1         | 1     | 1     | 0         | 0         | 0         | X 1            | X 1   | X 1   |

FF0: output = A

FF1: output = B

FF2: output = C

Custom 3-bit synchronous counter k-maps

| A\BC | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0    | 0  | 0  | 1  | 0  |
| 1    | X  | X  | X  | X  |

$$J_A = (B)(C)$$

| A\BC | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0    | X  | X  | X  | X  |
| 1    | 1  | 1  | 1  | 1  |

$$K_A = (1)$$

| A\BC | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0    | 0  | 1  | X  | X  |
| 1    | 0  | 0  | X  | X  |

$$J_B = (A')(C)$$

| A\BC | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0    | X  | X  | 1  | 0  |
| 1    | X  | X  | 1  | 1  |

$$K_B = (A + C)$$


| A\BC | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0    | 1  | X  | X  | 1  |
| 1    | 0  | X  | X  | 0  |

$JC = (A')$

| A\BC | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0    | X  | 1  | 1  | X  |
| 1    | X  | 1  | 1  | X  |

$KC = (1)$

 *Custom 3-bit synchronous counter state diagram*



## QUESTIONS

### Questions from the Experiment


**What is a synchronous counter?**

- The term synchronous refers to events that have a fixed time relationship with each other. A synchronous counter is one which all the flip-flops in the counter are clocked at the same time by a common clock pulse.

**Applications of the synchronous counter?**

### A Digital Clock

A common example of a counter application is in timekeeping systems. Figure 9-48 is a simplified logic diagram of a digital clock that displays seconds, minutes, and hours. First, a 60 Hz sinusoidal ac voltage is converted to a 60 Hz pulse waveform and divided down to a 1 Hz pulse waveform by a divide-by-60 counter formed by a divide-by-10 counter followed by a divide-by-6 counter. Both the *seconds* and *minutes* counts are also produced by divide-by-60 counters, the details of which are shown in Figure 9-49. These counters count from 0 to 59 and then recycle to 0; synchronous decade counters are used in this particular implementation. Notice that the divide-by-6 portion is formed with a decade counter with a truncated sequence achieved by using the decoder count 6 to asynchronously clear the counter. The terminal count, 59, is also decoded to enable the next counter in the chain.

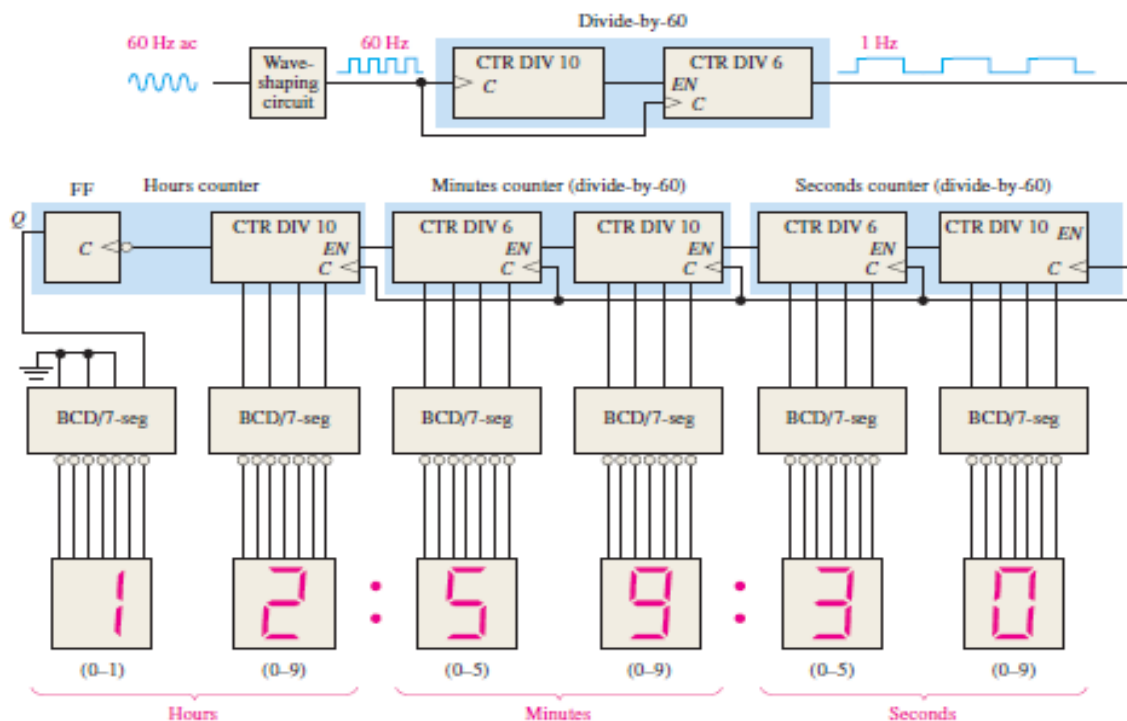

**FIGURE 9-48** Simplified logic diagram for a 12-hour digital clock. Logic details using specific devices are shown in Figures 9-49 and 9-50.

The *hours* counter is implemented with a decade counter and a flip-flop as shown in Figure 9-50. Consider that initially both the decade counter and the flip-flop are RESET, and the decode-12 gate and decode-9 gate outputs are HIGH. The decade counter advances through all of its states from zero to nine, and on the clock pulse that recycles it from nine back to zero, the flip-flop goes to the SET state ( $J = 1, K = 0$ ). This illuminates a 1 on the tens-of-hours display. The total count is now ten (the decade counter is in the zero state and the flip-flop is SET).



counters. Note that the outputs are in binary order (the right-most bit is the LSB).



inputs and outputs, the right-most bit is the LSB.

to one rather than back to zero.

Source: *Digital Fundamentals, Eleventh Edition, Thomas L. Floyd, 2015.*