

Lab#2 Operational Amplifier

Leonardo Fusser (1946995)

Objectives:

- Design a non-inverting voltage amplifier
- Take voltage and current measures on the amplifier
- Test the limits of the amplifier

Material: Simulated on Mindi

To hand in to Team Assignment

- 1- This document with the answers and measures. Copy-paste screenshots when required.
- 2- You provide comments to all screenshots
- 3- Upload the wxsch project file



Lab preparation: Fill in the calculate column for all tables

Lab work


Part 1: Non-inverting amplifier

In this part of the lab, you are going to build a non-inverting op-amp based amplifier to amplify an AC signal.


Wire the following circuit:

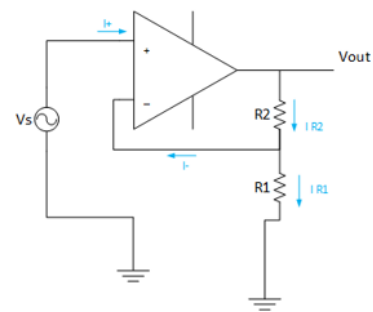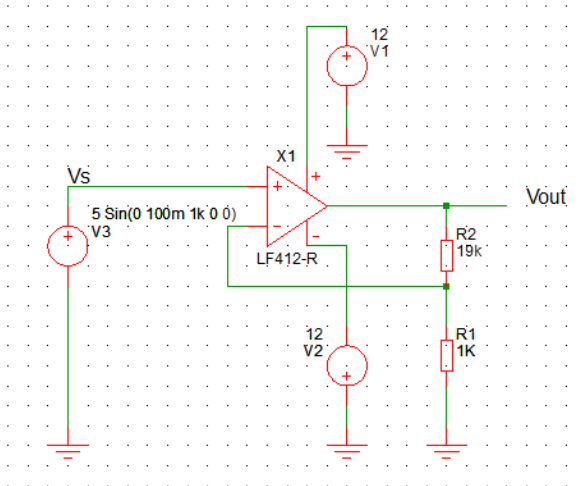

Set Vs to 200mV peak:

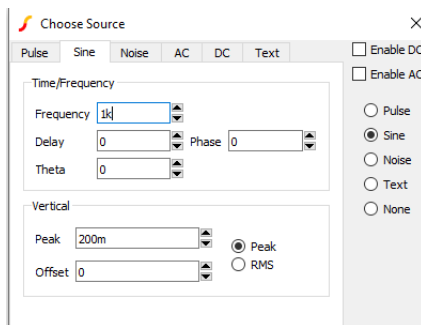

Run the simulator for at least 2 cycles:

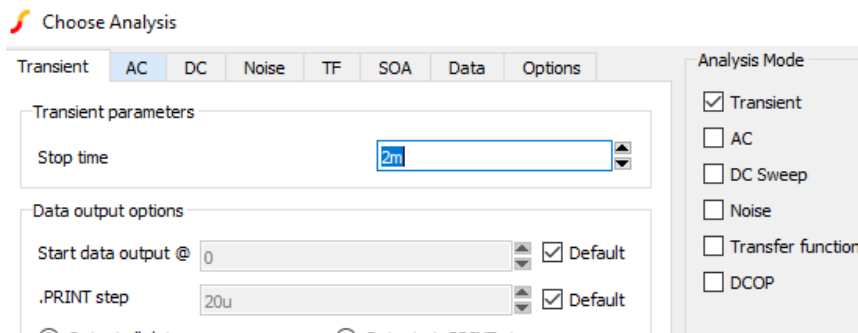


Fill up the following table. The grey area should be calculated.

To measure peak values:

1. Undock the Waveform Viewer
2. Waveform Viewer -> Measure -> Maximum
3. Select all measures

	Measures	Calculations
V _S peak	199.96771mV	200mV
V _{out} peak	3.9983515V	$V_{R1}(p) + V_{R2}(p) = 3.79843399V + 199.91751mV$
V _{R1} peak	199.91751mV	$I_{R2}(p) * R2 = 198.9782uA * 1K = 198.9782mV$
V _{R2} peak	3.79843399V	$V_{out}(p) - V_{R2}(p) = 3.9983515V - 199.91751mV$
A _{cl}	~20	$V_{out}(p) / V_{s}(p) = 3.9983515V / 199.96771mV$
I _{R2} peak	198.97804uA	$V_{R1}(p) / R1 = 3.79843399V / 19K\Omega = 199.917uA$
I _{R1} peak	198.9782uA	$V_{R2}(p) / R2 = 199.91751mV / 1K\Omega = 199.917uA$
I ₋ peak	4.5141708nA	N/A

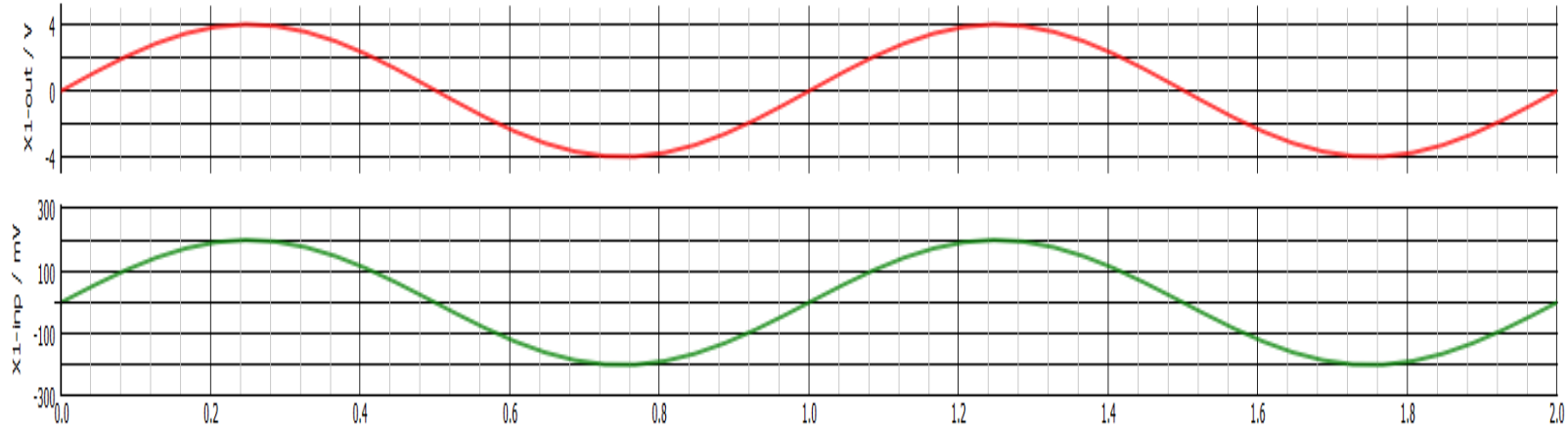Take a screenshot of V_s and V_{out} waveforms stacked on top of one another.



Red waveform: V_{out} & Green waveform: V_s . $V_{out} = \sim 4V_p$ & $V_s = \sim 200mV_p$


Part 2: Vout max

In this section you will look at the effect of connecting a load to the circuit. Then you are going to increase V_s and see whether V_{out} reaches its maximum value.

Keeping V_s at 200mV peak, load the output with a 30 Ohm value.

Run the simulator and take a screenshot of V_s and V_{out} waveforms on top of one another.

Explain the V_{out} waveform.

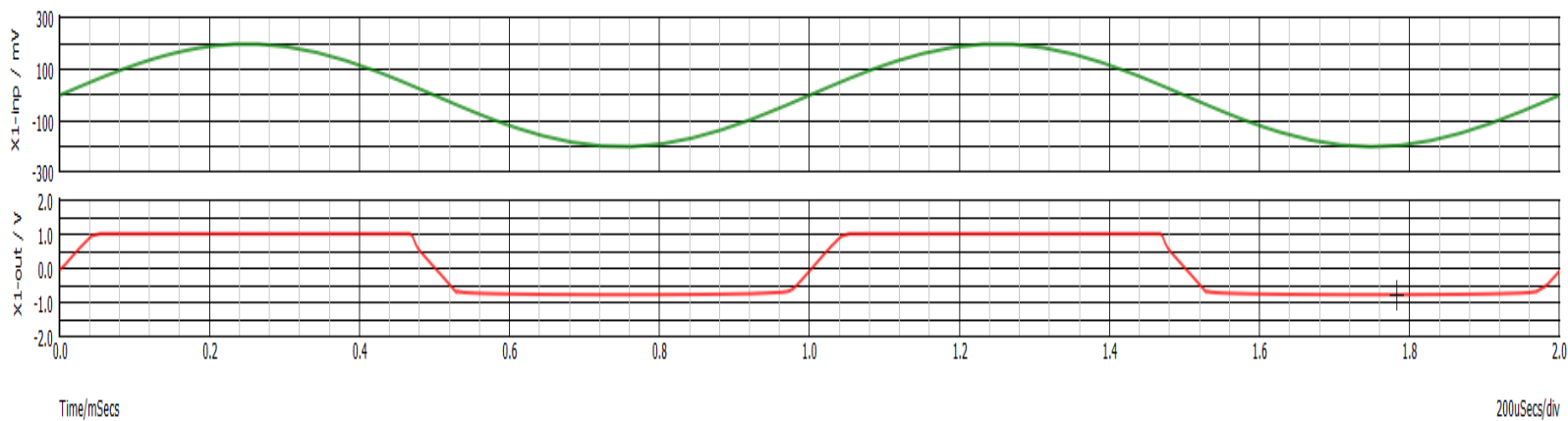

Red waveform: V_{out} & Green waveform: V_s . $V_{out} = \sim 1V_p$ & $V_s = \sim 200mV_p$. Above is a good example when the Op-Amp is in "protection mode". The load connected to the Op-Amp is too much to handle causing the V_{out} signal to look saturated. The Op-Amp is limiting the load to 1Vp to prevent damage to the Op-Amp itself. Below are calculations for further explanation.

From that waveform find $I_{o\ max}$ in source mode for this Op-Amp? Explain

We can observe the maximum tolerable output current of the Op-Amp by calculating as follows:


$$I_{O(MAX)} = \frac{1V_p}{30\Omega} = \sim 33.3mA$$

From the calculation above, we can see that the maximum amount of current that the Op-Amp can source is around 33mA. Any possible increase in current can possibly damage the Op-Amp or any other components in the circuit. "Source mode" is the opposite term to "sink/sink mode" where the Op-Amp is providing the power to power the load connected to the output of the Op-Amp.

Now, remove the load from the circuit. Then increase V_{in} to 1 Volt peak.

Run the simulator and take a screenshot of V_s and V_{out} waveforms stacked on top of one another.

Explain the V_{out} waveform.

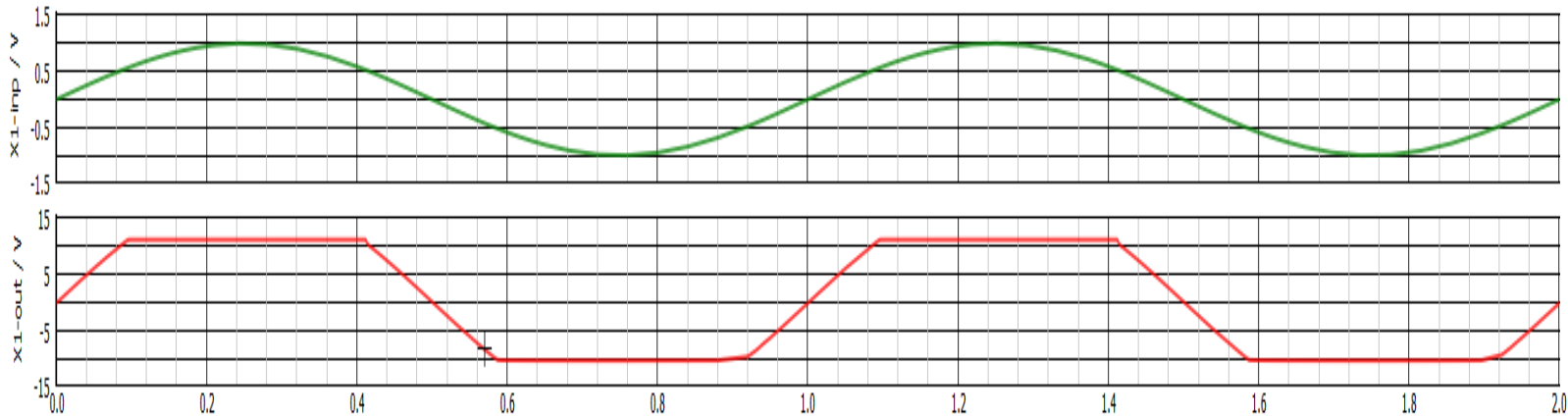

Red waveform: V_{out} & Green waveform: V_s . $V_{out} = \sim 10V_p$ & $V_s = \sim 1V_p$. Above is a good example when there is no load connected to the output of the Op-Amp. The output of the Op-Amp looks saturated because the Op-Amp is limiting the output from exceeding its supply voltage. This phenomenon can be expressed as follows:

$$\begin{aligned} +V_{OUT(MAX)} &= V_{CC} - 2V \\ -V_{OUT(MAX)} &= -V_{CC} + 2V \end{aligned}$$

Substituting for our values yields:

$$\begin{aligned} +V_{OUT(MAX)} &= 12V - 2V = +10V_p \\ -V_{OUT(MAX)} &= -12V + 2V = -10V_p \end{aligned}$$


These values can be seen in the above screenshot.

You must give a demo before leaving the classroom.

After lab questions

Compare I_o max measured with the datasheets. Data LF412 datasheets are uploaded in Teams.

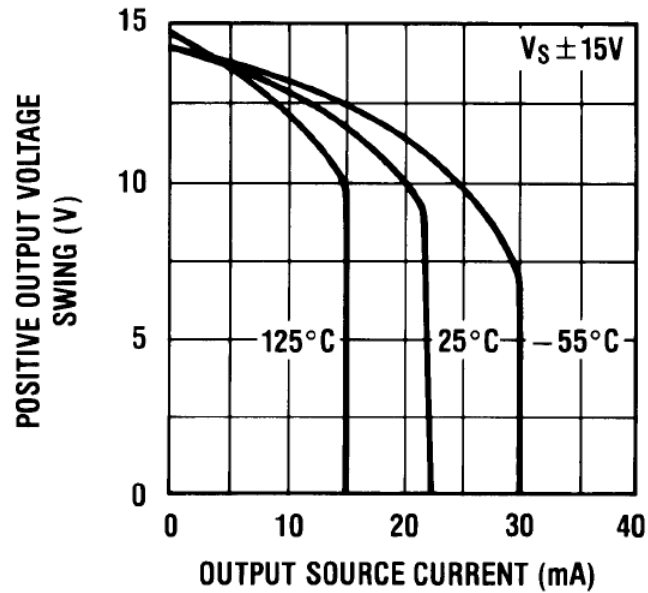The maximum output current that was calculated from above shows that the Op-Amp can tolerate loads up to around 33mA. Looking at the LF412's datasheet, we can see the suggested maximum tolerable output current:



Based on the information provided from the datasheet above, the suggested maximum output current this Op-Amp can handle is anywhere from 0mA to 30mA depending on ambient environment.