

# **Computer Circuit Fundamentals (Lab 5)**

*More complex experiments with Logic Gates*

**Leonardo Fusser, 1946995**

Experiment Performed on **4 October 2019**  
Report Submitted on **18 October 2019**

**Department of Computer Engineering Technology**  
*Computer Circuit Fundamentals*  
**Subash Handa**

## **TABLE OF CONTENTS**

Objectives .....	3
Design .....	3
Schematics.....	4
Questions.....	7

## OBJECTIVES

- Use NAND gates to implement AND, OR and NOT functions.
- Use NOR gates to implement AND, OR and NOT functions.
- To further understand Boolean logic/algebra.
- To further enhance understanding with ICs.
- To further enhance understanding with logic gates.

## DESIGN

### *Part 1 Experiment*

- **Part 1** experiment consisted of logic implementation of basic gates with NAND or NOR gates. Part 1a consisted of implementing AND, OR and NOT gates using only NAND gates (refer to Question 1a logic diagrams under “Schematics” for reference and for logic circuit diagrams and truth tables). Part 1b consisted of implementing AND, OR and NOT gates using only NOR gates (refer to Question 1b logic diagrams under “Schematics” for reference and for logic circuit diagrams and truth tables).

### *Part 2 Experiment*

- **Part 2** experiment consisted of logic implementation of a Boolean expression **using NAND gates**. This Boolean expression ( $F = AB'C' + A'BC' + A'B'C + ABC$ ) was simplified to  $(A + B + C)$  which is similar to an **XOR expression**. With this simplified expression, a logic circuit was created *using only NAND gates* and that circuit was tested with the simplified expression (Refer to Question 2 logic diagram under “Schematics” for reference and for logic circuit diagram and truth table).

### *Part 3 Experiment*

- **Part 3** experiment consisted of logic implementation of a Boolean expression **using NOR gates**. This Boolean expression ( $F = AB'C' + A'BC' + A'B'C + ABC$ ) was simplified to  $(A + B + C)$  which is similar to an **XOR expression**. With this simplified expression, a logic circuit was created *using only NOR gates* and that circuit was tested with the simplified expression (Refer to Question 3 logic diagram under “Schematics” for reference and for logic circuit diagram and truth table).

### *Part 4 Experiment*


- **Part 4** experiment consisted of creating a logic circuit diagram of a 3-input majority gate (otherwise known as a 3-input AND gate) **using only NAND gates**. The circuit was tested based on the logic of an AND gate. (Refer to Question 4 logic diagram under “Schematics” for reference and for logic circuit diagram and truth table).

## SCHEMATICS

### Question 1a logic diagram

Simulating an AND gate using a NAND gate


Input		Output
A	B	$F = A.B$
0	0	0
0	1	0
1	0	0
1	1	1

 

### Question 1a logic diagram


Simulating a NOT (inverter) gate using a NAND gate

A	NOT A
0	1
1	0

 


### Question 1a logic diagram

Simulating an OR gate using a NAND gate

 


Inputs		Output
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

 

### Question 1b logic diagram

Simulating an AND gate using a NOR gate


Input		Output
A	B	$F = A.B$
0	0	0
0	1	0
1	0	0
1	1	1

 

**Question 1b logic diagram**


Simulating a NOT (inverter) gate using a NOR gate

A	NOT A
0	1
1	0

 


**Question 1b logic diagram**


Simulating an OR gate using a NOR gate

 

Inputs		Output
A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1

 


**Question 2 Logic Diagram**

 

3-input XOR gate			
A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


### Question 3 Logic Diagram

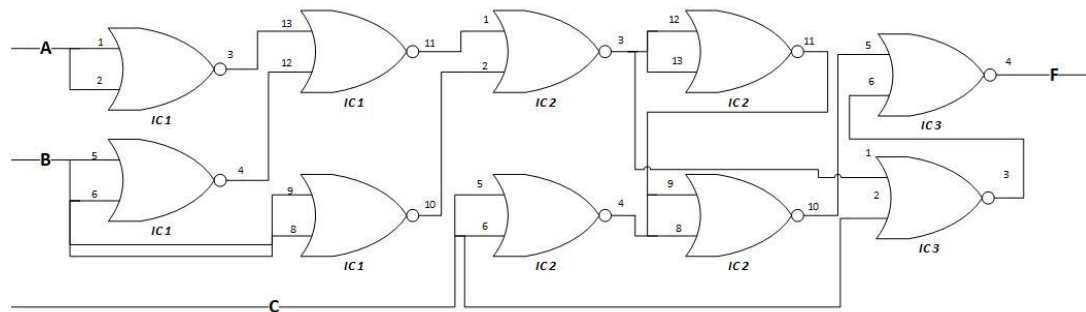


3-input XOR gate

A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

### Question 4 Logic Diagram

 

### 3 Input AND Gate

 

TRUTH TABLE

INPUTS			OUTPUT
W	X	Y	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

**QUESTIONS*****For Part 1***

- A: AND, OR and NOT gates were implemented only using NAND gates. A logic circuit diagram was created along with a truth table proving the logic (refer to Part 1 experiment under “Design” for reference).
- B: AND, OR and NOT gates were implemented only using NOR gates. A logic circuit diagram was created along with a truth table proving the logic (refer to Part 1 experiment under “Design” for reference).

***For Part 2, Part 3, Part 4***

- A: All circuits were wired and logic diagrams were developed based on those circuits.
- B: All circuits were tested and the logic was debugged if any issues were present.
- C: The instructor verified the logic for all circuits.  
(refer to Part 2, Part 3 and Part 4 experiment under “Design” for reference)