

# **AC: series RC circuits (Lab 4)**

*More on capacitors and RC circuits*

**Leonardo Fusser, 1946995**

Experiment Performed on **13 February 2020**  
Report Submitted on **26 February 2020**

**Department of Computer Engineering Technology**  
*Circuit Analysis & Simulation II*  
*Day Yann Fong, Manijeh Khataie, Andreea Iftimie*

**VANIER**  
C É G E P / C O L L E G E  
Learning today Leading tomorrow

## **TABLE OF CONTENTS**

1.0 Purpose.....	3
2.0 Equipment Needed.....	3
3.0 Pre-Lab.....	3
4.0 Experiemntal Results .....	5
5.0 Questions.....	12
6.0 Conclusion .....	12

## 1.0 PURPOSE

- To observe current and voltage relationships in a series RC circuit.
- To measure phase angles in a series RC circuit.

## 2.0 EQUIPMENT NEEDED

- (1x) desktop waveform generator.
- (3x) 4-band (1/4 watt) resistors.
- (1x) non-polarized capacitors.
- (1x) electronics breadboard.
- (1x) Keysight oscilloscope.
- (? x) BNC cables, oscilloscope accessories and others.

## 3.0 PRE-LAB

### *Prelab work*

1. Refer to the circuit of Figure 1. For each value of R, calculate the theoretical values for the quantities listed in Table 1, assuming  $V_g$  is at  $0^\circ$ .

For the quantity listed as “phase”, calculate the phase angle between generator current and generator voltage. If the current leads the voltage, the angle is negative, indicating the circuit is capacitive. This angle will be the same as the angle of impedance.

*\*Voltages represented in this table are in RMS.*

R	(1.8 k $\Omega$ )	(5.6 k $\Omega$ )	(12 k $\Omega$ )
Z	<b>8.2K<math>\Omega</math></b>	<b>9.7K<math>\Omega</math></b>	<b>14.2K<math>\Omega</math></b>
$I_G$	<b>367<math>\mu A</math></b>	<b>308<math>\mu A</math></b>	<b>211<math>\mu A</math></b>
$V_R$	<b>661mV</b>	<b>1.72V</b>	<b>2.534V</b>
$V_C$	<b>2.92V</b>	<b>2.45</b>	<b>1.68V</b>
Phase	<b>-77°</b>	<b>-54°</b>	<b>-32°</b>

Table 1: Series RC circuit calculation

*\*Calculations on next page*

**Calculations:**

(for 1.8kΩ)

Calculated  $X_C$ :

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi(2kHz)(10nF)}$$

$$X_C = 7.9k\Omega$$

Calculated Z:

$$Z = \sqrt{X_C^2 + R^2}$$

$$Z = \sqrt{7.9k\Omega^2 + 1.8k\Omega^2}$$

$$Z = 8.2k\Omega$$

Calculated  $I_G$ :

$$I_G = \frac{V_G}{Z}$$

$$I_G = \frac{3.0V_{RMS}}{8.2k\Omega}$$

$$I_G = 367\mu A$$

Calculated  $V_R$ :

$$V_R = I_G * R$$

$$V_R = 367\mu A * 1.8k\Omega$$

$$V_R = 661mV_{RMS}$$

Calculated  $V_C$ :

$$V_C = I_G * X_C$$

$$V_C = 367\mu A * 7.9k\Omega$$

$$V_C = 2.92V_{RMS}$$

Calculated Phase:

$$Phase = \tan^{-1}\left(\frac{X_C}{R}\right)$$

$$Phase = \tan^{-1}\left(\frac{7.9k\Omega}{1.8k\Omega}\right)$$

$$Phase = -77^\circ$$

(for 5.6kΩ)

Calculated  $X_C$ :

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi(2kHz)(10nF)}$$

$$X_C = 7.9k\Omega$$

Calculated Z:

$$Z = \sqrt{X_C^2 + R^2}$$

$$Z = \sqrt{7.9k\Omega^2 + 5.6k\Omega^2}$$

$$Z = 9.7k\Omega$$

Calculated  $I_G$ :

$$I_G = \frac{V_G}{Z}$$

$$I_G = \frac{3.0V_{RMS}}{9.7k\Omega}$$

$$I_G = 308\mu A$$

Calculated  $V_R$ :

$$V_R = I_G * R$$

$$V_R = 308\mu A * 5.6k\Omega$$

$$V_R = 1.72V_{RMS}$$

Calculated  $V_C$ :

$$V_C = I_G * X_C$$

$$V_C = 308\mu A * 7.9k\Omega$$

$$V_C = 2.45V_{RMS}$$

Calculated Phase:

$$Phase = \tan^{-1}\left(\frac{X_C}{R}\right)$$

$$Phase = \tan^{-1}\left(\frac{7.9k\Omega}{5.6k\Omega}\right)$$

$$Phase = -54^\circ$$

(for 12kΩ)

Calculated  $X_C$ :

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi(2kHz)(10nF)}$$

$$X_C = 7.9k\Omega$$

Calculated Z:

$$Z = \sqrt{X_C^2 + R^2}$$

$$Z = \sqrt{7.9k\Omega^2 + 12k\Omega^2}$$

$$Z = 14.2k\Omega$$

Calculated  $I_G$ :

$$I_G = \frac{V_G}{Z}$$

$$I_G = \frac{3.0V_{RMS}}{14.2k\Omega}$$

$$I_G = 211\mu A$$

Calculated  $V_R$ :

$$V_R = I_G * R$$

$$V_R = 211\mu A * 12k\Omega$$

$$V_R = 2.53V_{RMS}$$

Calculated  $V_C$ :

$$V_C = I_G * X_C$$

$$V_C = 211\mu A * 7.9k\Omega$$

$$V_C = 1.68V_{RMS}$$

Calculated Phase:

$$Phase = \tan^{-1}\left(\frac{X_C}{R}\right)$$

$$Phase = \tan^{-1}\left(\frac{7.9k\Omega}{12k\Omega}\right)$$

$$Phase = -32^\circ$$

2a, b)

**Questions:**

- ✓ 1. If capacitance were increased in a series RC circuit, would impedance increase or decrease? Explain your answer.
- ✓ 2. If the frequency applied to a series RC circuit were decreased, would the magnitude of the angle of impedance be larger or smaller? Explain your answer.
- ✓ 3. For each of the 3 cases in Table 2, calculate the circuit phase angle using the measured voltages and the following relationship. Comment on your calculated results compared to measured phases.

*Q 2a+2b:*  
*Impedance and Phase*

$\theta = -\tan^{-1} \frac{V_C}{V_R}$

$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi (2.0 \text{ kHz}) (10 \text{ nF})}$   
 $X_C = 7.9 \text{ k}\Omega$

Phasor diagrams showing:  
 - A vector diagram for impedance:  $Z = R \angle 0^\circ + X_C \angle -90^\circ = 14.2 \text{ k}\Omega \angle -32^\circ$   
 - A phasor diagram for voltages:  $V_R$  and  $V_C$  are in phase with  $I_R$  and  $I_C$  respectively, with  $V_C$  lagging  $V_R$  by  $90^\circ$ .

Circuit Analysis and Simulation II DY Fong © 2020 Page 3

## 4.0

### EXPERIMENTAL RESULTS

*Results from the Procedure section:*

- 3) Connect the circuit of the following figure, using 1.8 k $\Omega$  as R. After the circuit is connected, set the generator voltage to 3.0V, at frequency of 2.0 kHz.

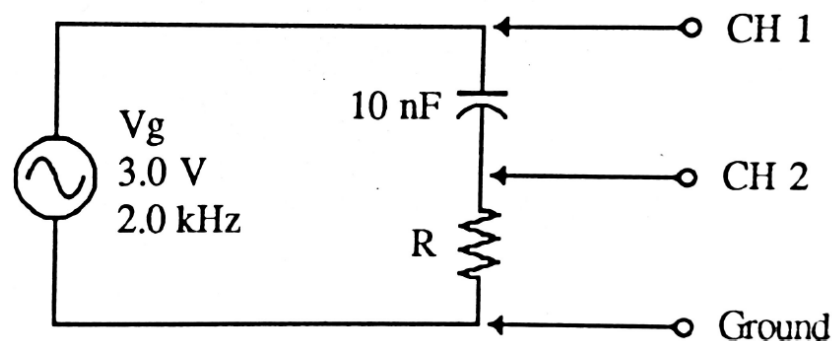


Figure 1 : Series RC measurement circuit

**Where:**


$R = 1.8 \text{ k}\Omega$  or  $5.6 \text{ k}\Omega$  or  $12 \text{ k}\Omega$

$V_G = 3.0 V_{\text{RMS}}$

$F = 2.0 \text{ kHz}$

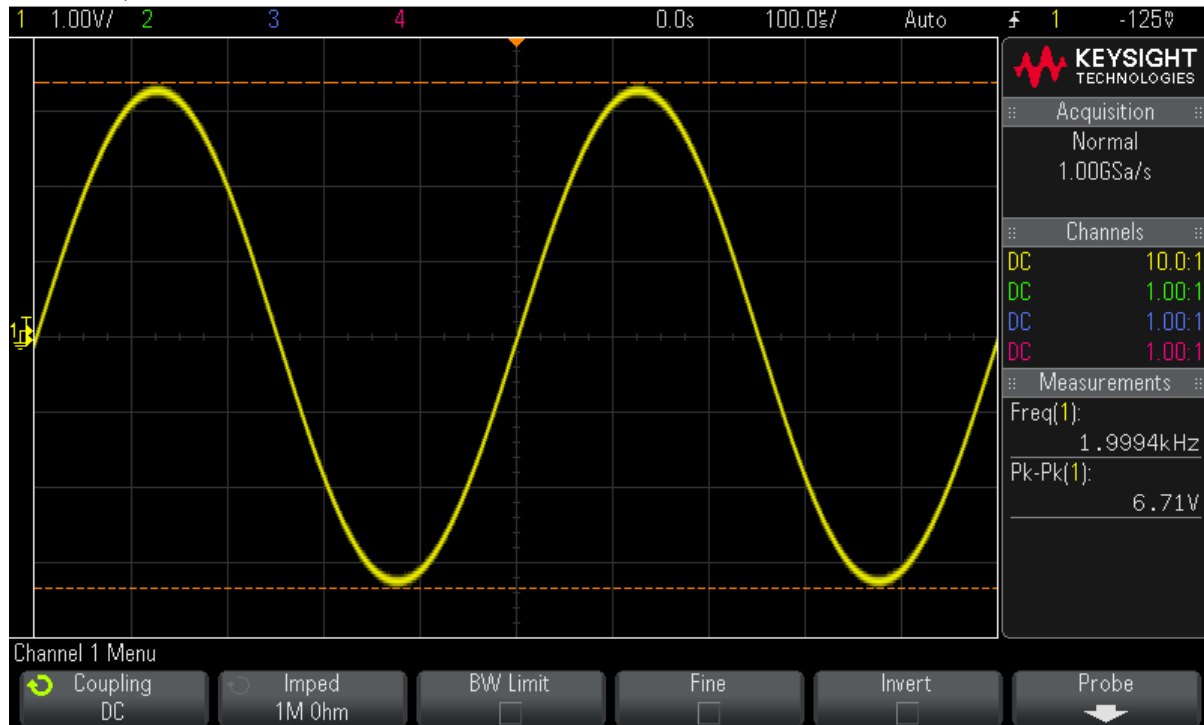
4)

MSO-X 3034A, MY54020421: Tue Feb 06 22:11:44 2018




Screenshot representing the voltage across the  $1.8k\Omega$  resistor ( $6.71V_{pp} = 524mV_{RMS}$  shown above)

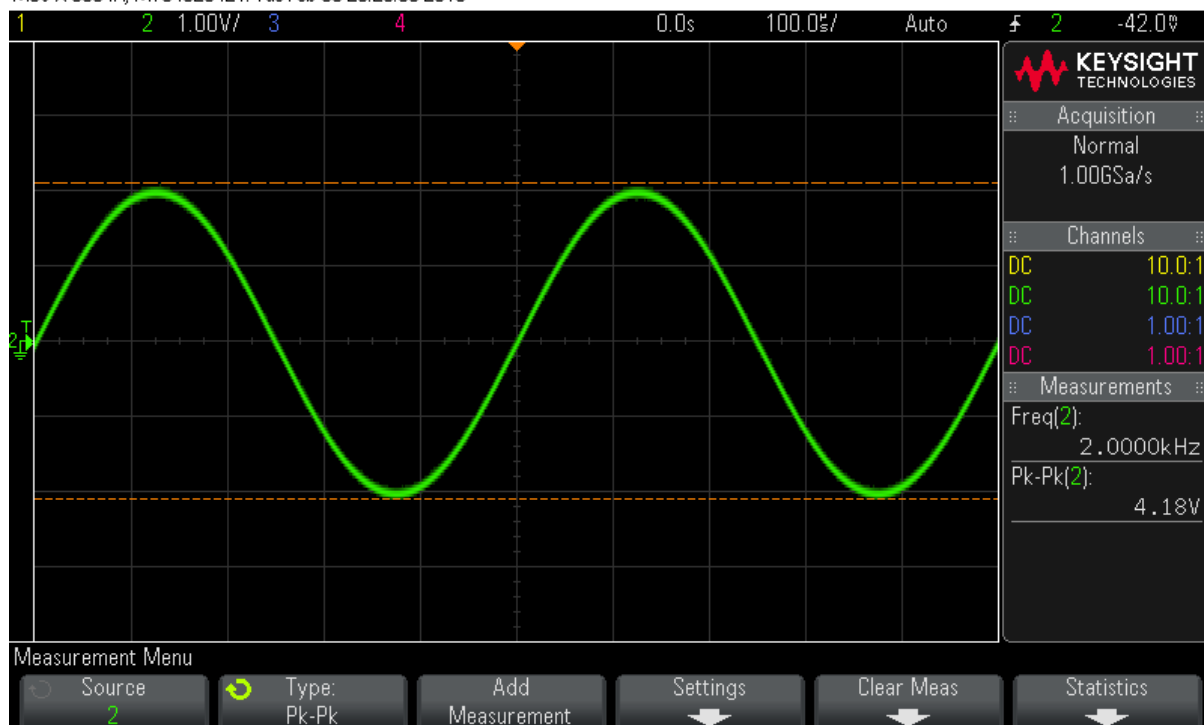MSO-X 3034A, MY54020421: Tue Feb 06 23:25:08 2018



Screenshot representing the voltage across the  $5.6k\Omega$  resistor ( $4.18V_{pp} = 1.46mV_{RMS}$  shown above)

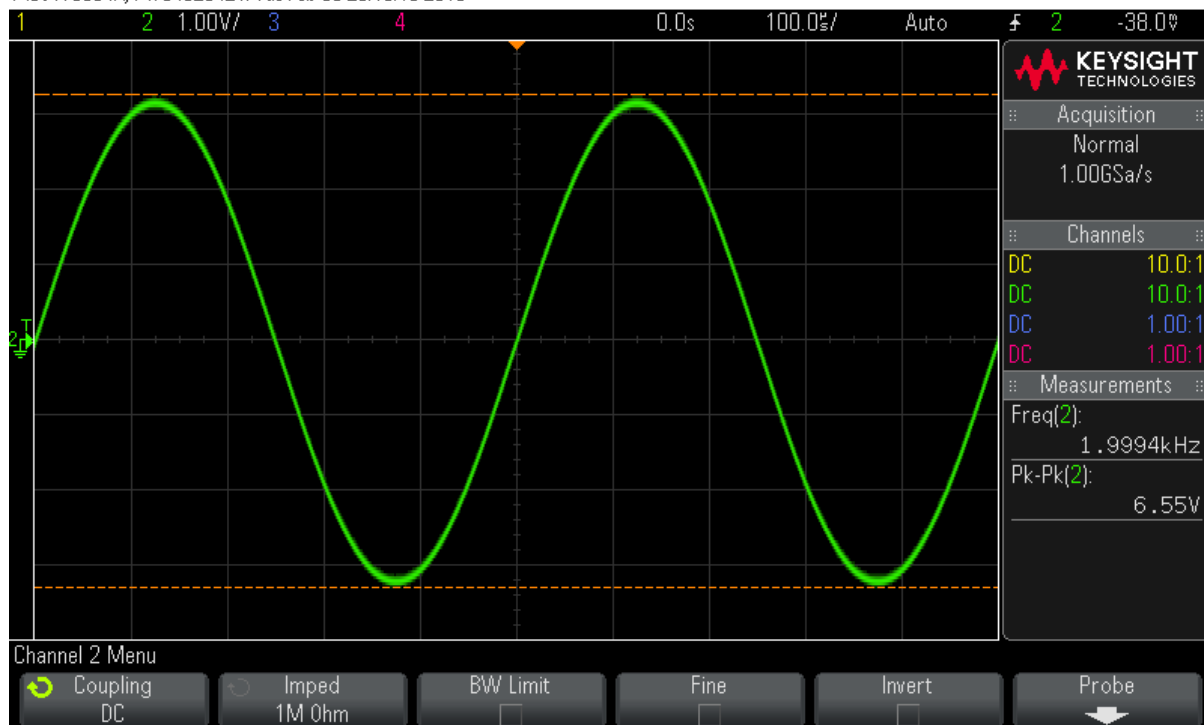MSO-X 3034A, MY54020421: Tue Feb 06 23:15:10 2018



Screenshot representing the voltage across the 12k $\Omega$  resistor ( $6.55V_{pp} = 2.31mV_{RMS}$  shown above)

5)


**Note:**

CH1-Yellow: Probe across 10nF capacitor (as shown in Question 3 schematic above).

CH2-Green: Probe across 1.8k $\Omega$  or 5.6k $\Omega$  or 12k $\Omega$  resistor (as shown in Question 3 schematic above).


*\*This applies to the screenshots in Question 5 and Question 6.*

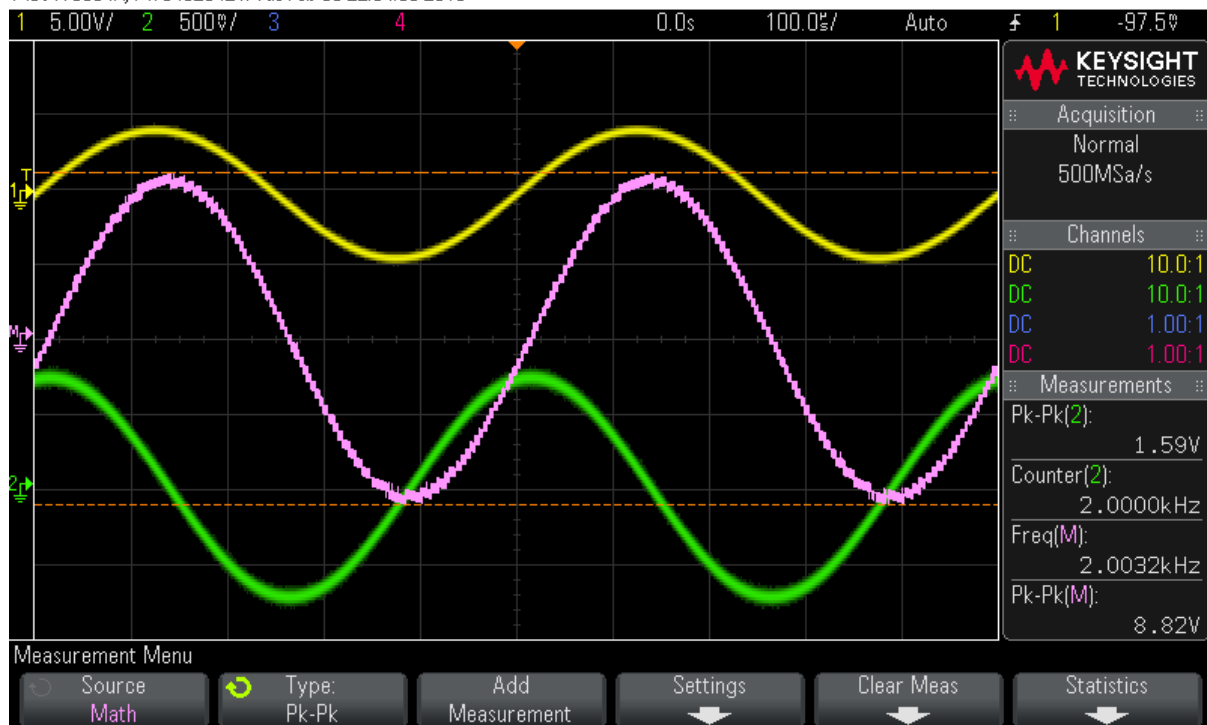MSO-X 3034A, MY54020421: Tue Feb 06 22:54:59 2018



The voltage across the 10nF capacitor (1.8kΩ circuit) ( $8.82V_{pp} = 3.12V_{RMS}$  shown above)

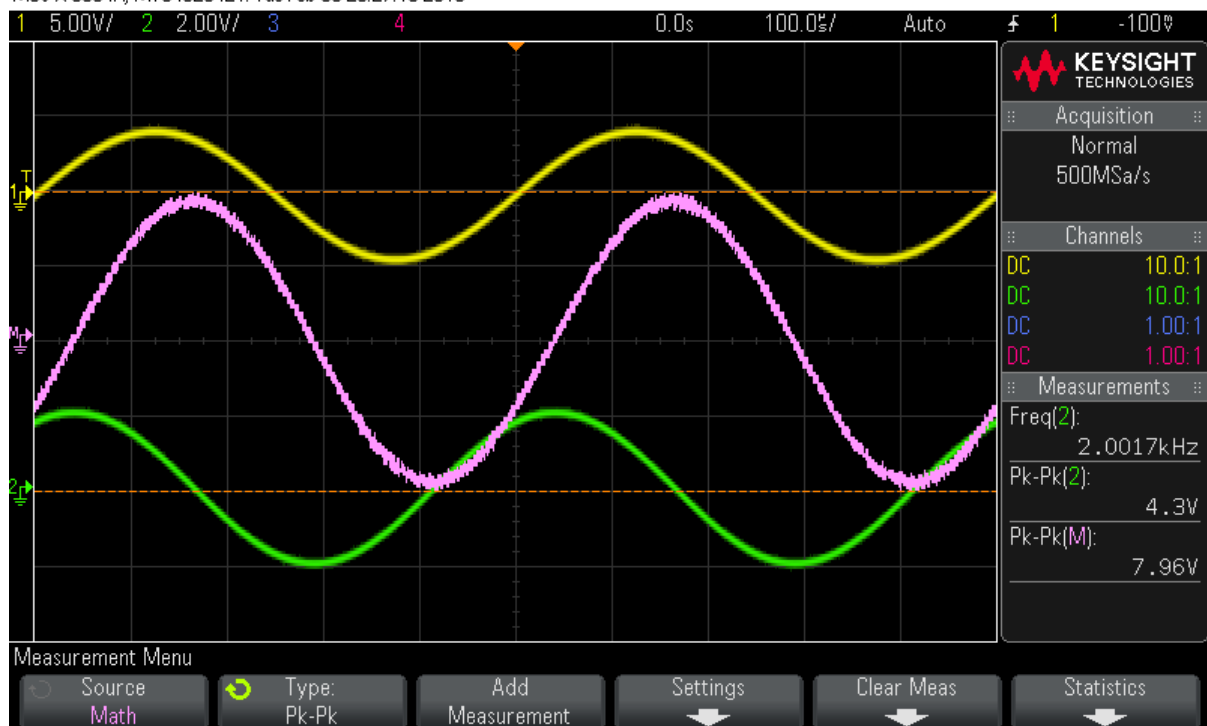
MSO-X 3034A, MY54020421: Tue Feb 06 23:27:15 2018



The voltage across the 10nF capacitor (5.6kΩ circuit) ( $7.96V_{pp} = 2.81V_{RMS}$  shown above)



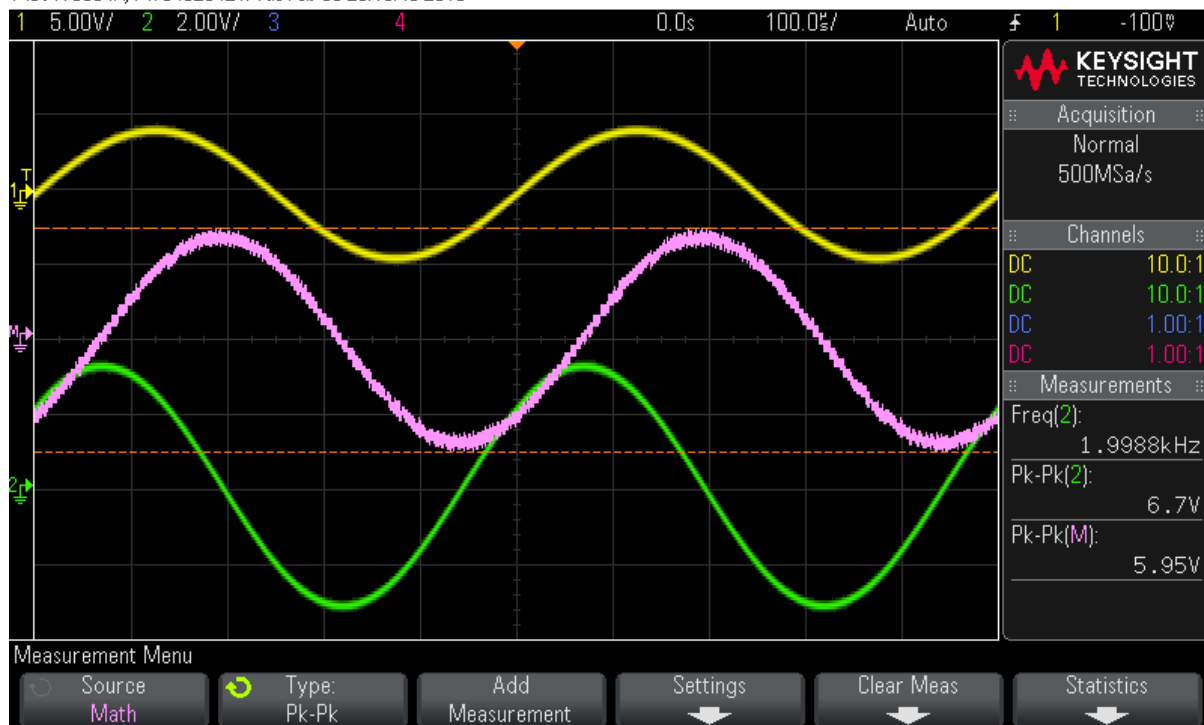
MSO-X 3034A, MY54020421: Tue Feb 06 23:18:48 2018



*The voltage across the 10nF capacitor (12kΩ circuit) ( $5.95V_{pp} = 2.10V_{RMS}$  shown above)*

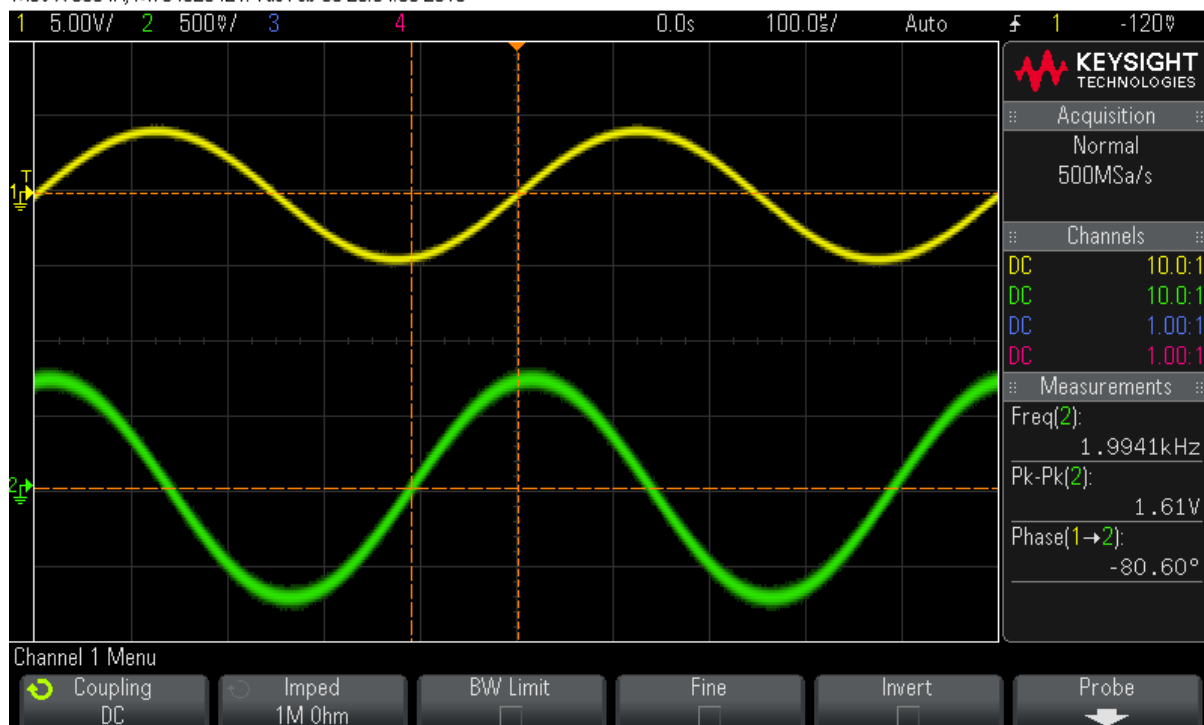
6) \*Refer to note in Question 5.

MSO-X 3034A, MY54020421: Tue Feb 06 23:34:50 2018




*Phase angle measurement for 10nF, 1.8kΩ circuit. The measured phase angle here is -80.60°.*

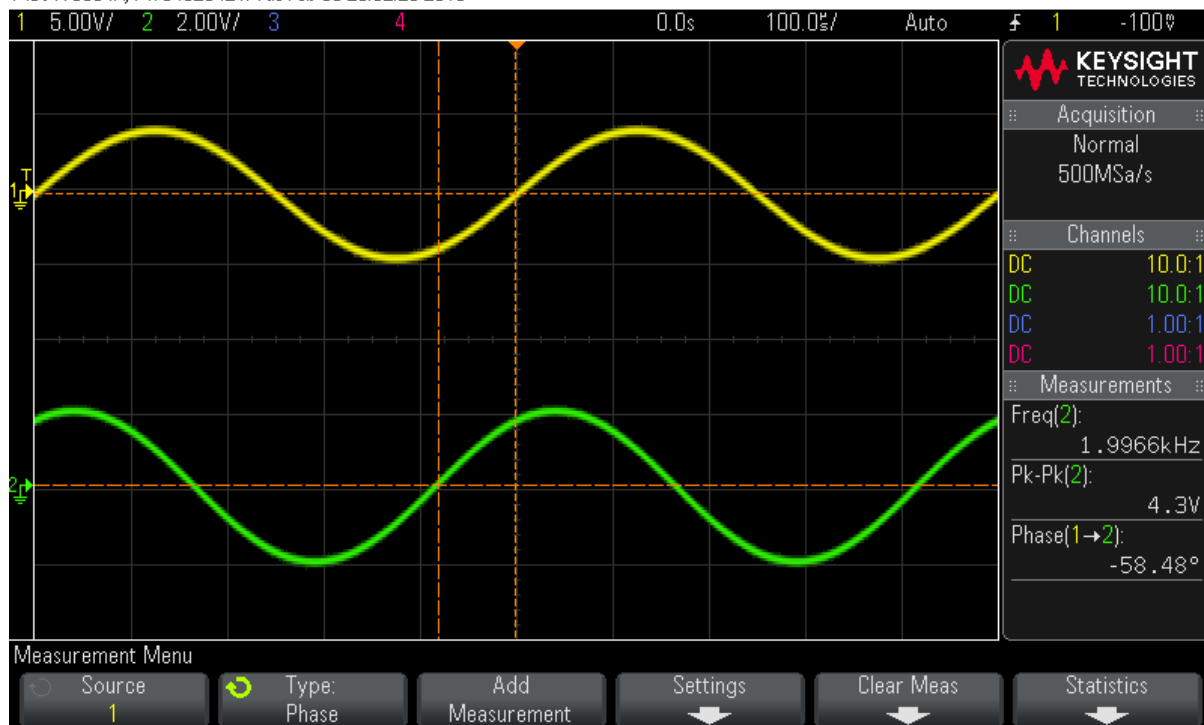MSO-X 3034A, MY54020421: Tue Feb 06 23:32:29 2018



Phase angle measurement for 10nF, 5.6kΩ circuit. The measured phase angle here is -58.48°.

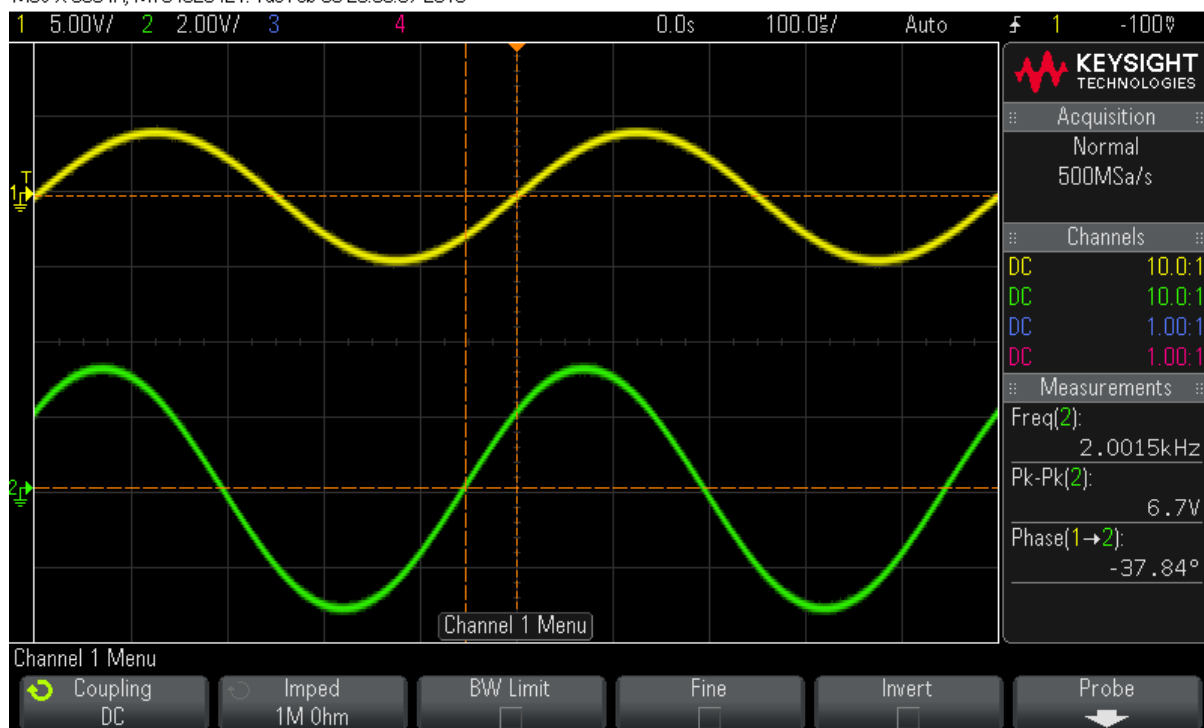MSO-X 3034A, MY54020421: Tue Feb 06 23:36:57 2018



Phase angle measurement for 10nF, 12kΩ circuit. The measured phase angle here is -37.84°.

Comment:

The measurement of the phase angle between the waveform generator voltage (CH1) and waveform generator current (CH2) wasn't too complicated to achieve. Using the measurement function on the scope and selecting "Phase" as the measurement, the phase difference between CH1 and CH2 resulted my measured phase angle.

7, 8, 9) Calculate the circuit impedance using the generator voltage and your calculated current.

R	1.8 kΩ	5.6 kΩ	12 kΩ
Measured $V_R$	<b>524mV<sub>RMS</sub></b>	<b>1.46V<sub>RMS</sub></b>	<b>2.31V<sub>RMS</sub></b>
Measured $V_C$	<b>3.12V<sub>RMS</sub></b>	<b>2.81V<sub>RMS</sub></b>	<b>2.10V<sub>RMS</sub></b>
Measured phase	<b>-80.60°</b>	<b>-57.90°</b>	<b>-37.26°</b>
Calculated $I_g$	<b>291μA</b>	<b>260μA</b>	<b>192μA</b>
Calculated Z	<b>10.3kΩ</b>	<b>11.5kΩ</b>	<b>15.6kΩ</b>

Table 2 : Series RC circuit measurements and calculations

**Calculations:**

(for 1.8kΩ)

(for 5.6kΩ)

(for 12kΩ)

Calculated  $I_g$ :

$$I = \frac{V_R}{R}$$

$$I = \frac{524mV_{RMS}}{1.8k\Omega}$$

$$\mathbf{I = 291\mu A}$$

Calculated  $I_g$ :

$$I = \frac{V_R}{R}$$

$$I = \frac{1.46V_{RMS}}{5.6k\Omega}$$

$$\mathbf{I = 260\mu A}$$

Calculated  $I_g$ :

$$I = \frac{V_R}{R}$$

$$I = \frac{2.31V_{RMS}}{12k\Omega}$$

$$\mathbf{I = 192\mu A}$$

Calculated Z:

$$Z = \frac{V_G}{I_g}$$

$$Z = \frac{3V_{RMS}}{291\mu A}$$

$$\mathbf{Z = 10.3k\Omega}$$

Calculated Z:

$$Z = \frac{V_G}{I_g}$$

$$Z = \frac{3V_{RMS}}{260\mu A}$$

$$\mathbf{Z = 11.5k\Omega}$$

Calculated Z:

$$Z = \frac{V_G}{I_g}$$

$$Z = \frac{3V_{RMS}}{192\mu A}$$

$$\mathbf{Z = 15.6k\Omega}$$

10)

- The circuit and demonstration were shown to the instructor (Manijeh Khataie) on February 13<sup>th</sup>, 2020.

## 5.0 QUESTIONS

---

- 1) *The impedance would decrease due to the value of  $X_C$ .*
- 2) *The magnitude RC of the angle of impedance would be larger because of the properties of  $X_C$ .*
- 3)  $R = 1.78k\Omega / \theta = 77.37^\circ$   
 $R = 5.59k\Omega / \theta = 54.91^\circ$   
 $R = 12.08k\Omega / \theta = 33.37^\circ$

*My calculated results compared to my measured phases are not exactly the same, but are within the accepted tolerance range.*

## 6.0 CONCLUSION

---

- Purpose of this lab has been achieved.
- Understood how to verify current and voltage relationships in a series RC circuit.
- Understood how to measure how to measure phase angles in a series RC circuit.