

Computational Logic Circuits (Online Lab 3)

Custom Sequencer

Leonardo Fusser, 1946995

Experiment Performed on **24 April 2020**
Report Submitted on **26 April 2020**

Department of Computer Engineering Technology
Computational Logic Circuits
Subash Handa

TABLE OF CONTENTS

Objectives	3
Design	3
Simulations	3

OBJECTIVES

- To understand the function of sequencers.
- To understand how to design a dual sequence sequencer.
- To verify and simulate the function of a 3-bit dual sequence sequencer.

DESIGN

Experiment


- There was one simulation done in this lab. We used the same fundamentals from the last lab. We were asked to create a dual sequence sequencer, where there was an even and odd cycle (an external mode switch was used to select which one). The sequence was in 3-bits so 3 JK flip-flops were used in the simulation. Proper design and testing were done as well. The simulations were done in "Logisim". Below outlines the work done in the lab.

SIMULATIONS

Simulations from the Experiment

Simulation made by: Leonardo Fusser (1946995)

For: Subash Handa
Computational Logic
Online Lab #3, Simulation 1

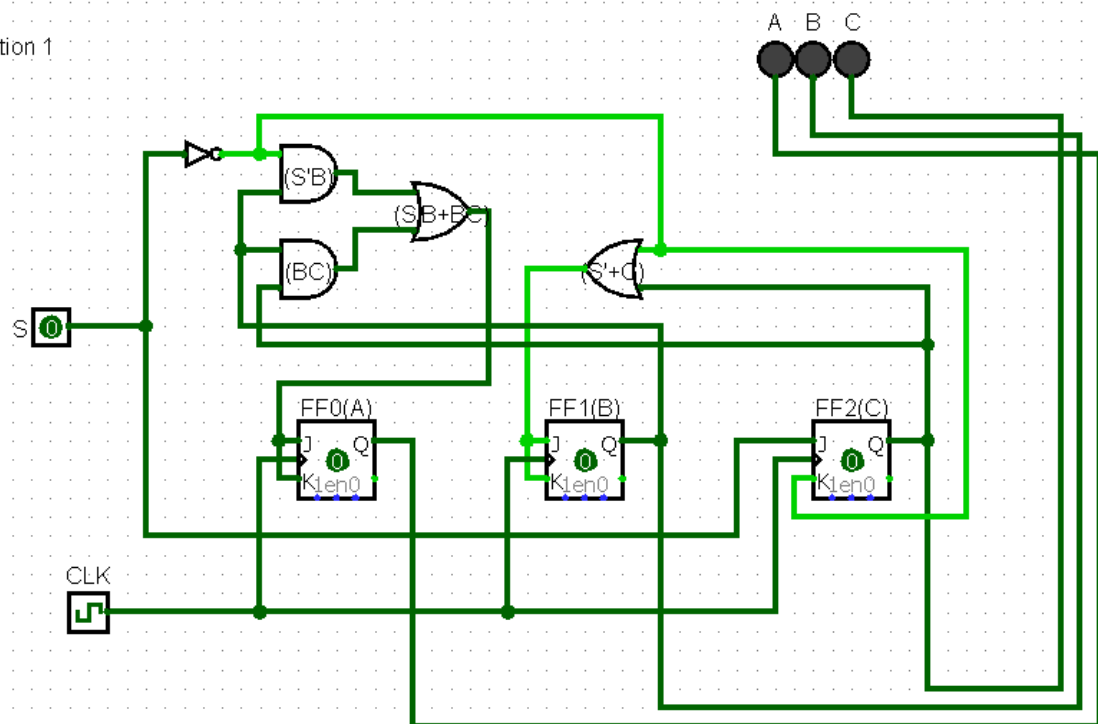

Custom 3-bit dual sequence sequencer simulation (above)

Custom 3-bit dual sequence sequencer transition table

Selector	(PRESENT)			(NEXT)			J-K Flip Flops		
	A _N	B _N	C _N	A _{N+1}	B _{N+1}	C _{N+1}	JA/KA	JB/KB	JC/KC
0	0	0	0	0	1	0	0 X	1 X	0 X
1	0	0	0	0	0	0	0 X	0 X	1 X
0	0	0	1	0	1	0	0 X	1 X	X 1
1	0	0	1	0	1	1	0 X	1 X	X 0
0	0	1	0	1	0	0	1 X	X 1	0 X
1	0	1	0	0	1	1	0 X	X 0	1 X
0	0	1	1	1	0	0	1 X	X 1	X 1
1	0	1	1	1	0	1	1 X	X 1	X 0
0	1	0	0	1	1	0	X 0	1 X	0 X
1	1	0	0	1	0	1	X 0	0 X	1 X
0	1	0	1	1	1	0	X 0	1 X	X 1
1	1	0	1	1	1	1	X 0	1 X	X 0
0	1	1	0	0	0	0	X 1	X 1	0 X
1	1	1	0	1	1	1	X 0	X 0	1 X
0	1	1	1	0	0	0	X 1	X 1	X 1
1	1	1	1	0	0	1	X 1	X 1	X 0

FF0: output = A

FF1: output = B

FF2: output = C

Custom 3-bit dual sequence sequencer k-maps

(S)A\BC	00	01	11	10
00	0	0	1	1
01	X	X	X	X
11	X	X	X	X
10	0	0	1	0

$$JA = (S'B + BC)$$

(S)A\BC	00	01	11	10
00	X	X	X	X
01	0	0	1	1
11	0	0	1	0
10	X	X	X	X

$$KA = (S'B + BC)$$

(S)A\BC	00	01	11	10
00	1	1	X	X
01	1	1	X	X
11	0	1	X	X
10	0	1	X	X

$$JB = (S' + C)$$

(S)A\BC	00	01	11	10
00	X	X	1	1
01	X	X	1	1
11	X	X	1	0
10	X	X	1	0

$$KB = (S' + C)$$

(S)A\BC	00	01	11	10
00	0	X	X	0
01	0	X	X	0
11	1	X	X	1
10	1	X	X	1

$$JC = (S)$$

(S)A\BC	00	01	11	10
00	X	1	1	X
01	X	1	1	X
11	X	0	0	X
10	X	0	0	X

$$KC = (S')$$

Custom 3-bit dual sequence sequencer state diagram

State diagram:

