

# **Computer Circuit Fundamentals (Lab 11)**

*MUXs and DeMUXs*

**Leonardo Fusser, 1946995**

Experiment Performed on **29 November 2019**  
Report Submitted on **29 November 2019**

Department of Computer Engineering Technology  
*Computer Circuit Fundamentals*  
*Subash Handa*

**VANIER**  
C É G E P / C O L L E G E  
Learning today Leading tomorrow

## **TABLE OF CONTENTS**

Objectives .....	3
Design .....	3
Schematics.....	3

## OBJECTIVES

- To understand how multiplexers function.
- To understand how demultiplexers function.
- To understand how to test and verify multiplexers and demultiplexers.
- To identify multiplexer chips (4-to-1 MUX: 74153, 1-to-4 deMUX: 74139).


## DESIGN

### Experiment


- First, we researched how multiplexers and demultiplexers function and how to identify them. Following that, there were two experiments conducted in this lab. The first one, to test a 4-to-1 MUX (74153) using the pencil box and to check results using a corresponding truth table. The second one, to test a 1-to-4 deMUX (74139) using the pencil box and to check results using a corresponding truth table. The tests were done during the lab period. Below shows the two circuits and their corresponding diagrams.

## SCHEMATICS

### 4-to-1 MUX

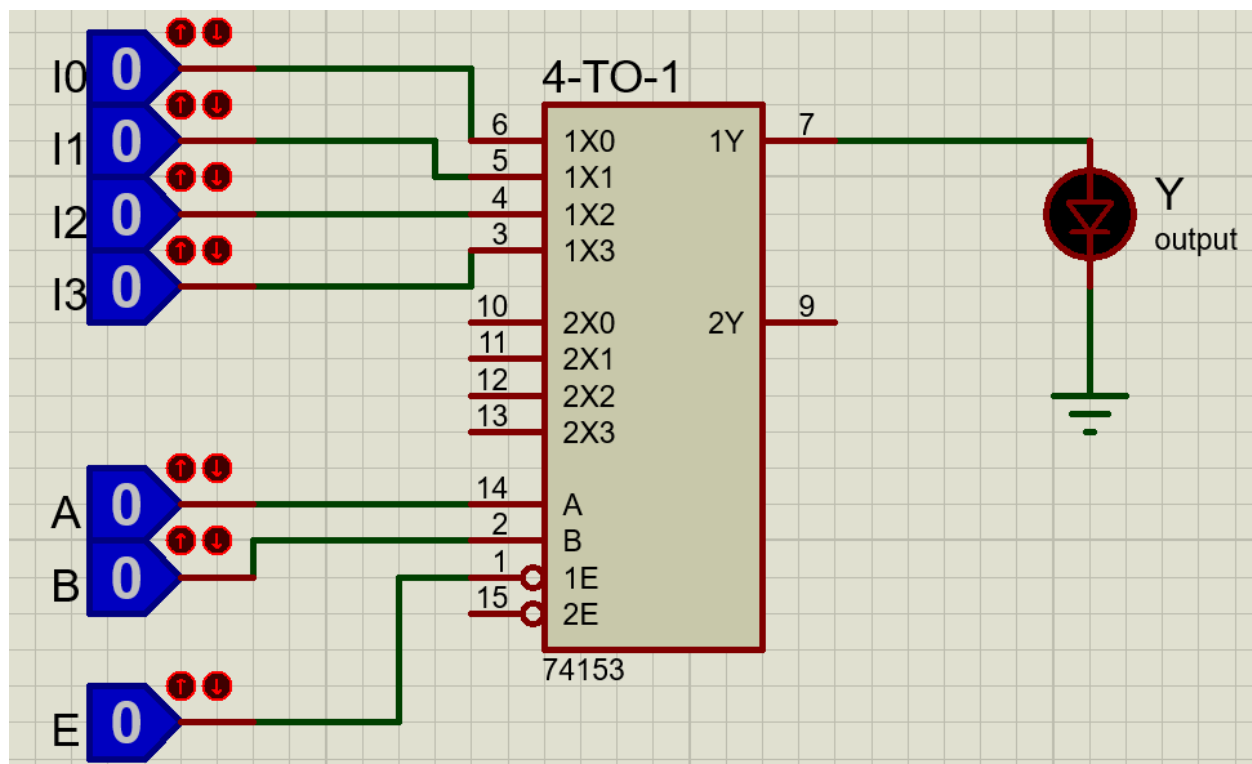

## Connection Diagram

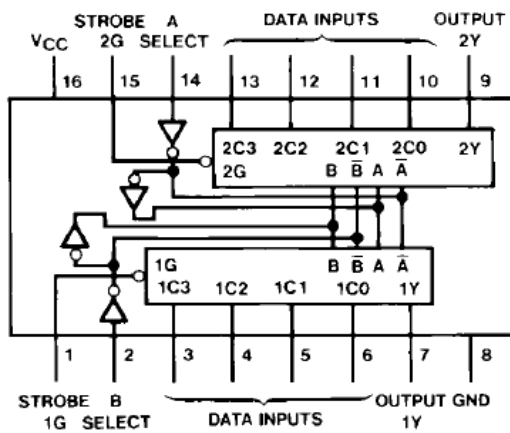

## Function Table

Select Inputs		Data Inputs				Strobe	Output
B	A	C0	C1	C2	C3	G	Y
X	X	X	X	X	X	H	L
L	L	L	X	X	X	L	L
L	L	H	X	X	X	L	H
L	H	X	L	X	X	L	L
L	H	X	H	X	X	L	H
H	L	X	X	L	X	L	L
H	L	X	X	H	X	L	H
H	H	X	X	X	L	L	L
H	H	X	X	X	H	L	H


Select inputs A and B are common to both sections.

H = HIGH Level

L = LOW Level


X = Don't Care

## 1-to-4 deMUX

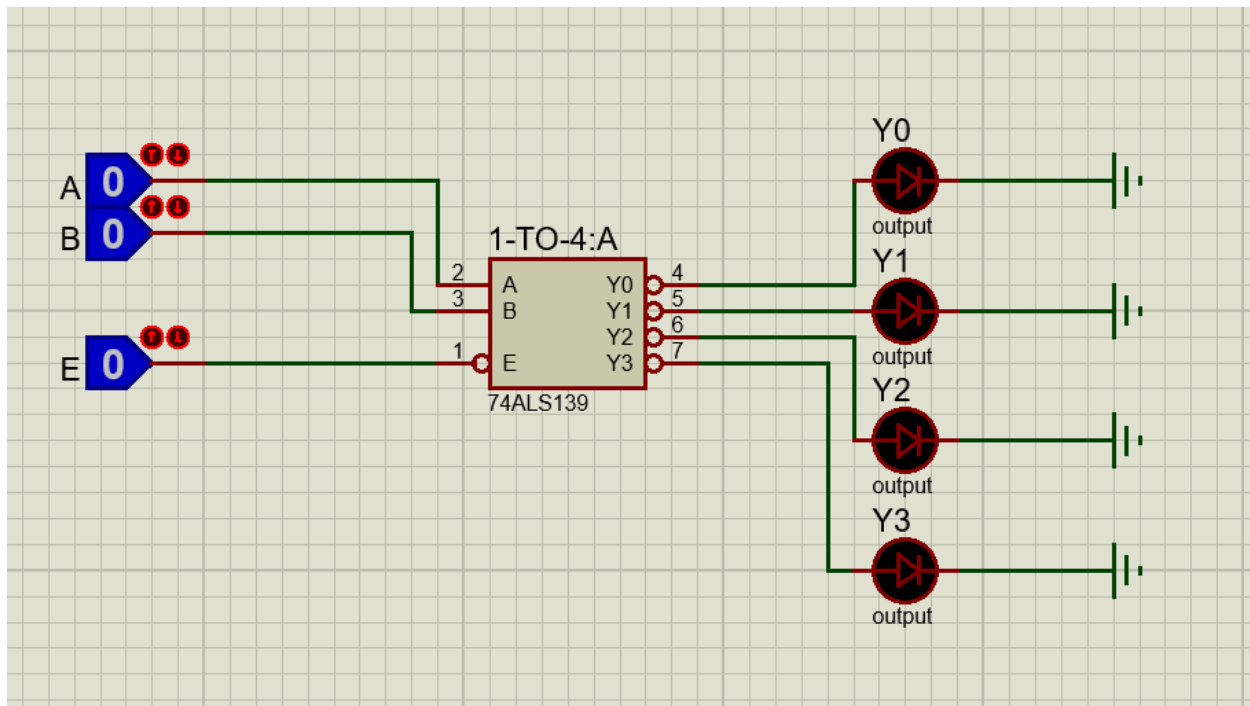

## 74139 2-Line-to-4-Line Decoder/Demultiplexer


74139

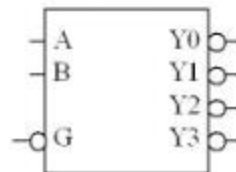

Enable	Select		Outputs			
G	B	A	Y0	Y1	Y2	Y3
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L
H	×	×	H	H	H	H

13

**74153**

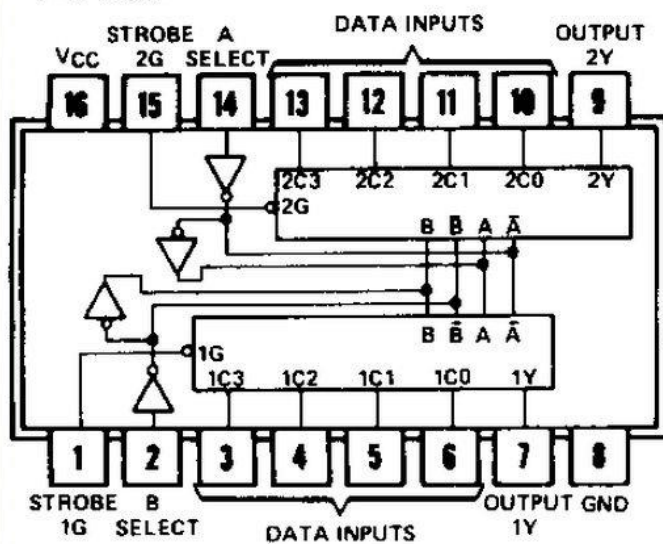

**74139**

