

Computational Logic Circuits (Lab 3)

zyBooks & subtractor circuit

Leonardo Fusser, 1946995

Experiment Performed on **14 February 2020**
Report Submitted on **21 February 2020**

Department of Computer Engineering Technology
Computational Logic Circuits
Subash Handa

TABLE OF CONTENTS

Objectives	3
Design	3
Schematics.....	3
Questions.....	3

OBJECTIVES

- To understand the topics covered in zyBooks for this week's lab.
- To understand how to use a 4-bit Full Adder IC to perform a subtraction operation.
- To understand how to effectively create Logic Circuits.

DESIGN

Experiment

- There were two parts in this lab. First, we asked to read from chapter 2.1, 2.2 and 3.1-3.5 in our zyBooks. Then, we had to compare two four-bit signed numbers, $X = x_3x_2x_1x_0$ and $Y = y_3y_2y_1y_0$ by using a subtractor circuit. The subtractor circuit was built using a 4-bit full adder IC (74LS83) to perform the operation $X - Y$. Finally, we had to determine the cases $X=Y$, $X<Y$, $X\leq Y$, $X>Y$ and $X\geq Y$.

SCHEMATICS

Schematics from the Experiment

The schematic for the subtractor logic-circuit is on the attached loose-leaf.

QUESTIONS

Questions from the Experiment

There are no questions that were asked for this lab.