
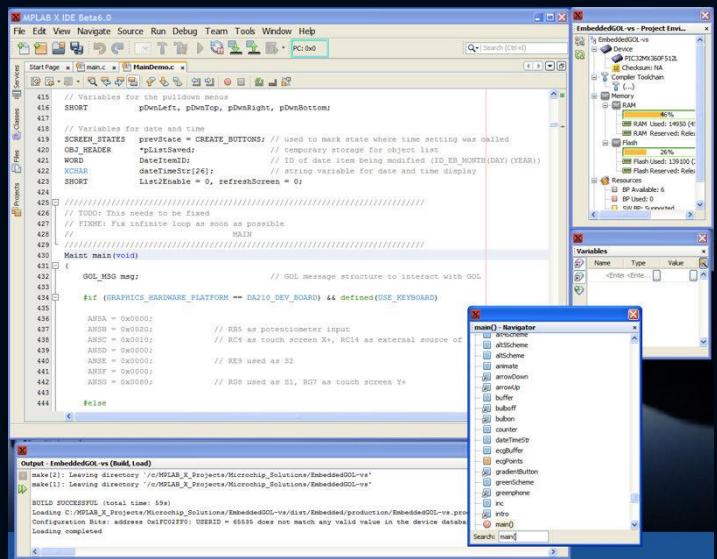



Lab Assignment Presentation

LEONARDO FUSSER (1946995)

Today's Topics:

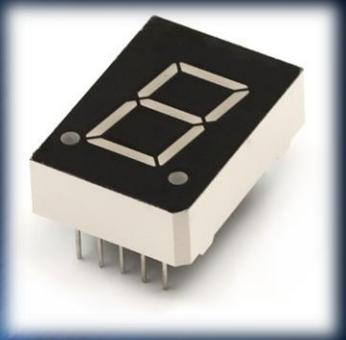- *Hardware overview & approach*
- *Software overview & approach*
- *Problems encountered & solutions*
- *What I learned & what I could improve*



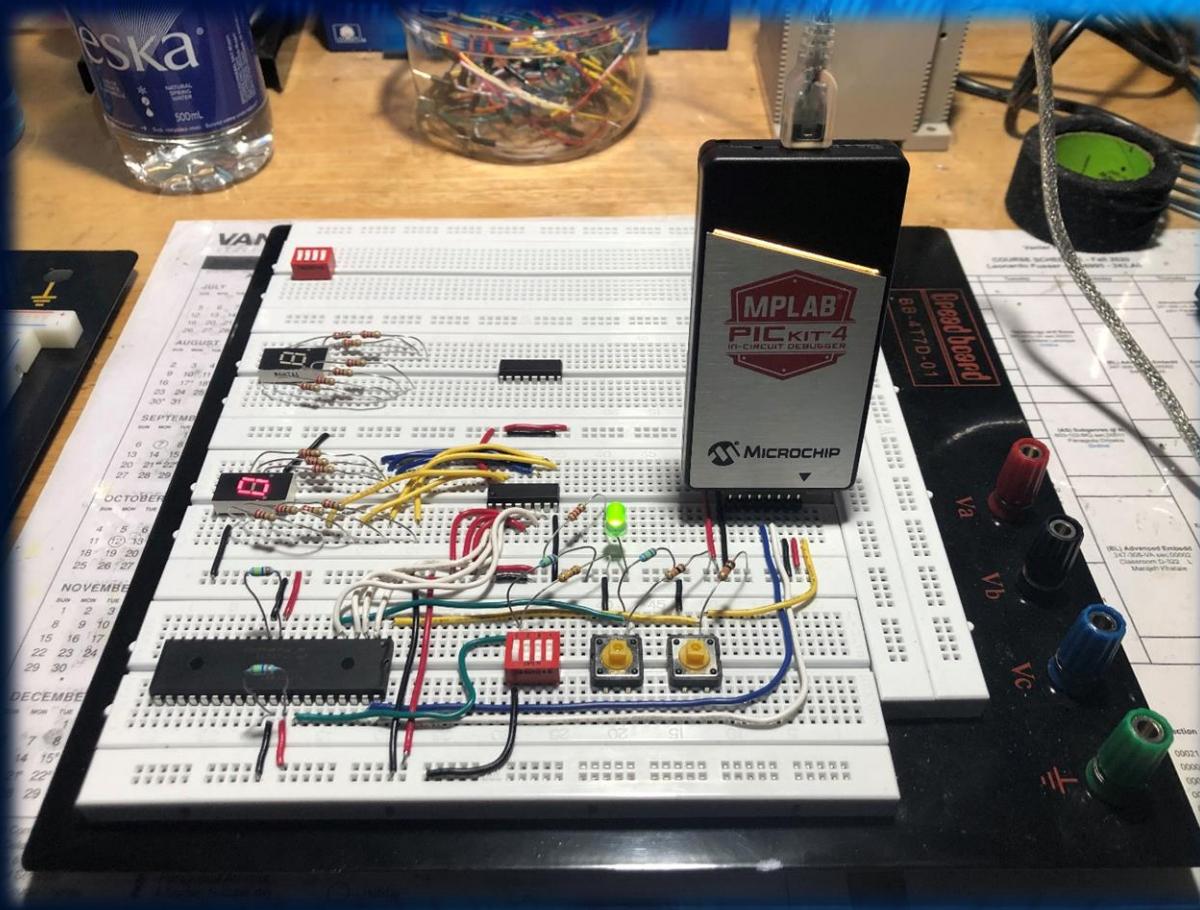


Hardware Overview

THE 7-SEGMENT DISPLAY, 7448 & DIP SWITCH INTERFACING TO PIC16F887

The 7448

Pin Arrangement

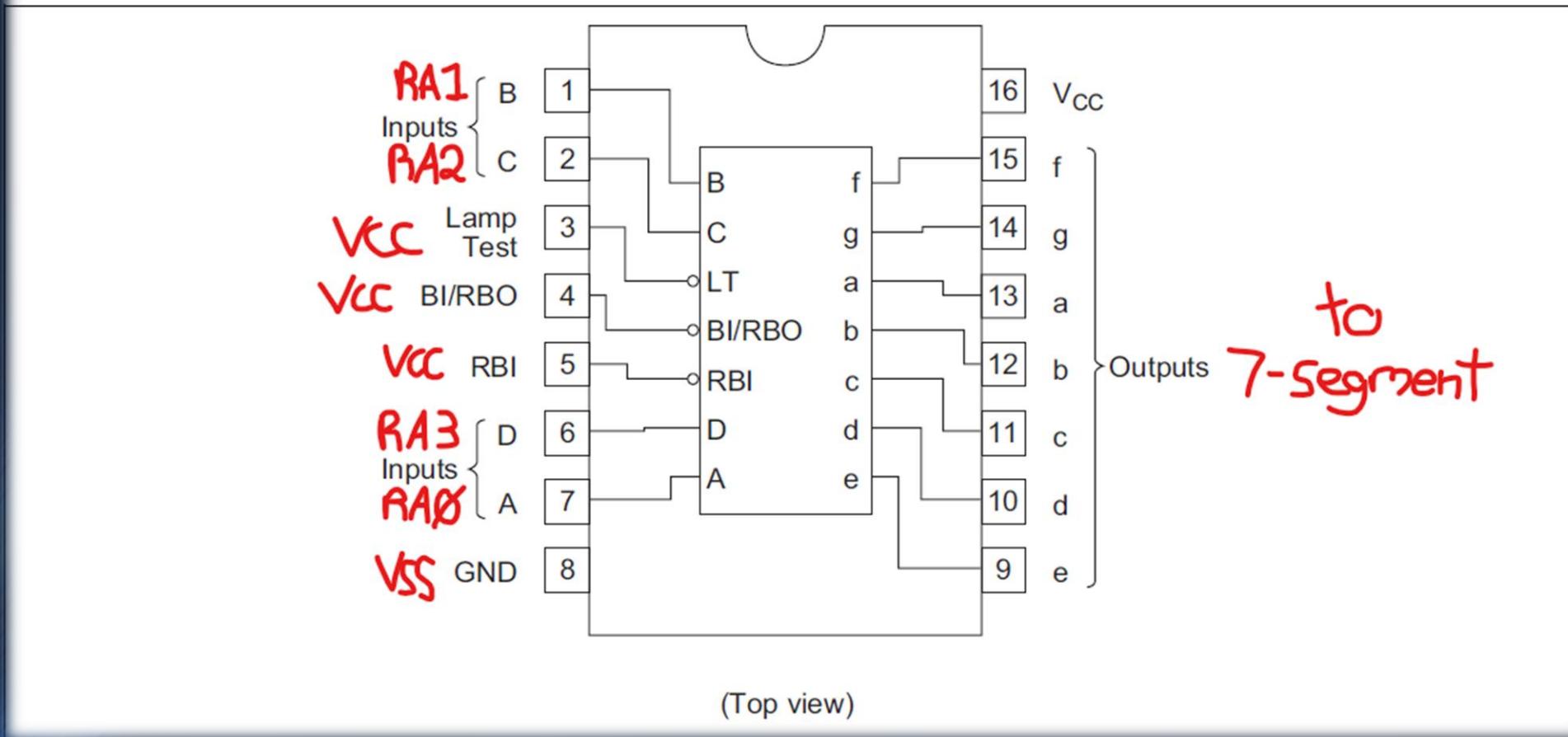


Connections to 7448 decoder/7-segment display driver


Function Table

Decimal or Function	Inputs						BI / RBO	Outputs							Note
	LT	RBI	D	C	B	A		a	b	c	d	e	f	g	
0	H	H	L	L	L	L	H	H	H	H	H	H	H	L	
1	H	X	L	L	L	H	H	L	H	H	L	L	L	L	
2	H	X	L	L	H	L	H	H	H	L	H	H	L	H	
3	H	X	L	L	H	H	H	H	H	H	H	L	L	H	
4	H	X	L	H	L	L	H	L	H	H	L	L	H	H	
5	H	X	L	H	L	H	H	H	L	H	H	L	H	H	
6	H	X	L	H	H	L	H	L	L	H	H	H	H	H	
7	H	X	L	H	H	H	H	H	H	H	L	L	L	L	
8	H	X	H	L	L	L	H	H	H	H	H	H	H	H	
9	H	X	H	L	L	H	H	H	H	H	L	L	H	H	1
10	H	X	H	L	H	L	H	L	L	L	H	H	L	H	
11	H	X	H	L	H	H	H	L	L	H	H	L	L	H	
12	H	X	H	H	L	L	H	L	H	L	L	L	H	H	
13	H	X	H	H	L	H	H	H	L	L	H	L	H	H	
14	H	X	H	H	H	L	H	L	L	L	H	H	H	H	
15	H	X	H	H	H	H	H	L	L	L	L	L	L	L	
BI	X	X	X	X	X	X	L	L	L	L	L	L	L	L	2
RBI	H	L	L	L	L	L	L	L	L	L	L	L	L	L	3
LT	L	X	X	X	X	X	H	H	H	H	H	H	H	H	4

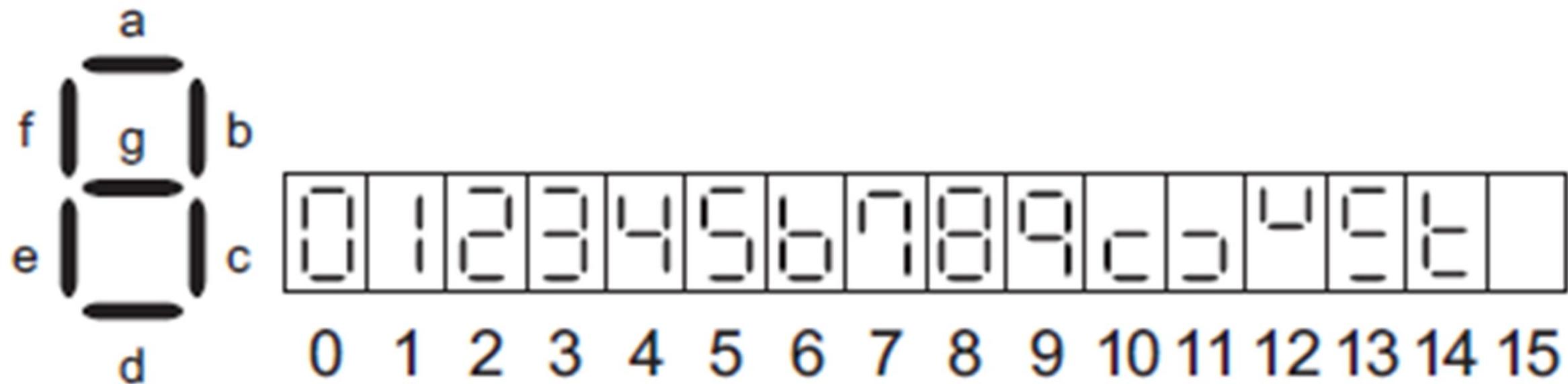
H: high level, L: low level, X: irrelevant



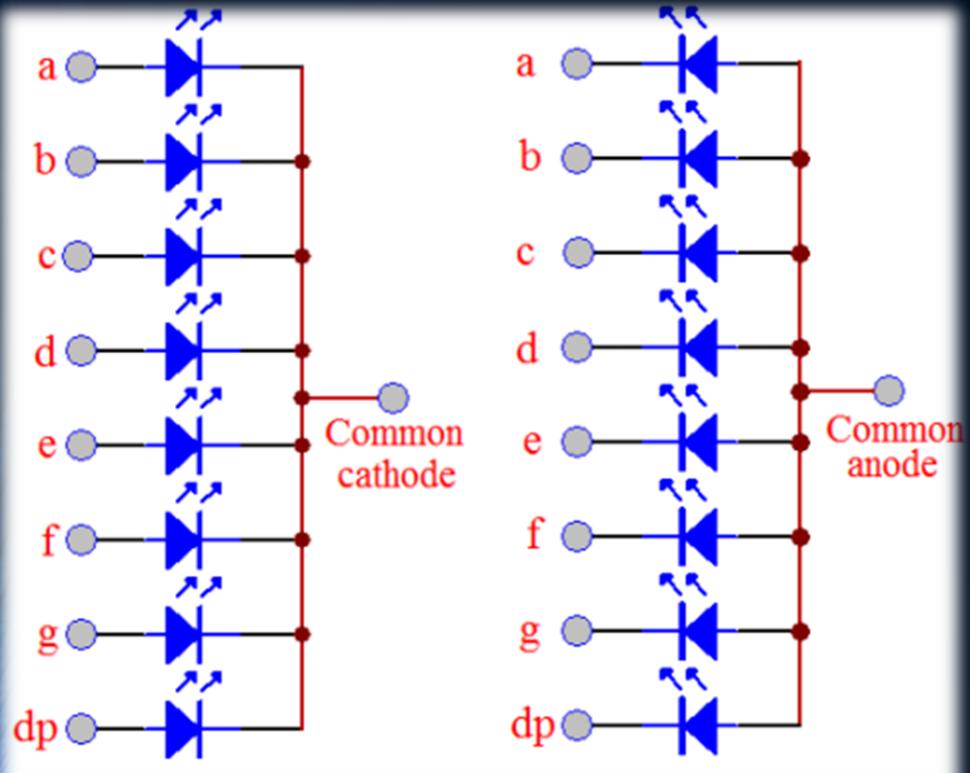Complete possible outputs on 7-segment display





Two types of segmented displays

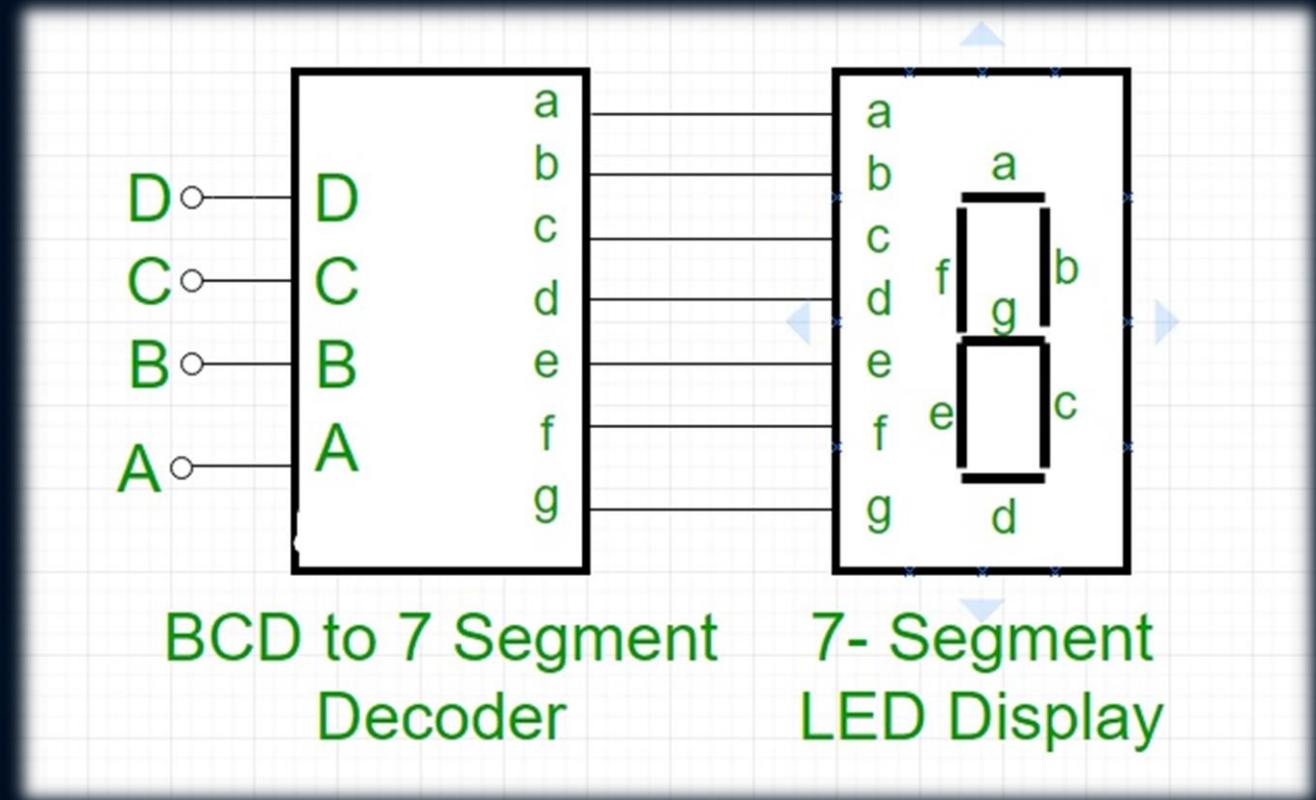

Typical hookup with common cathode 7-segment display

Complete Schematic

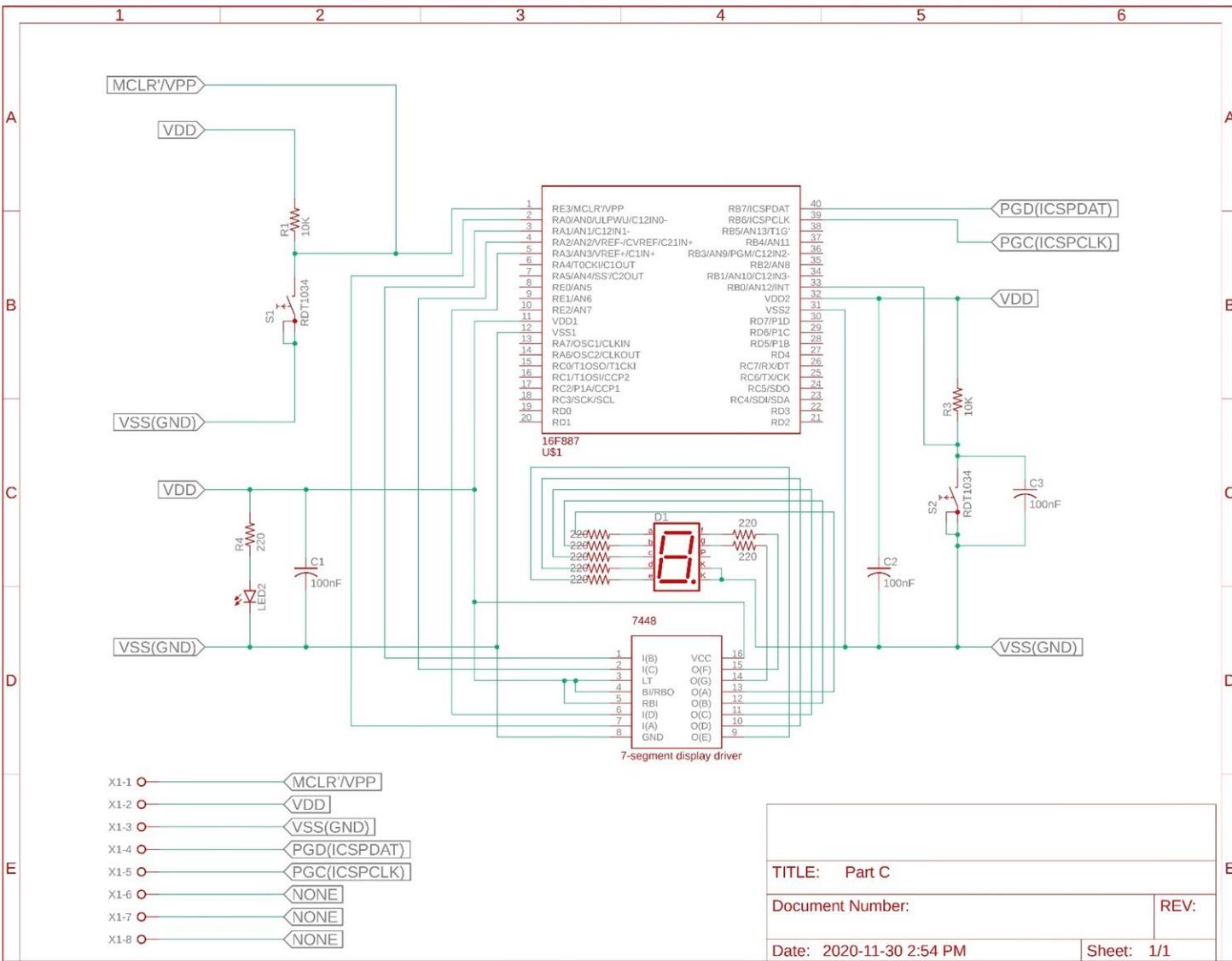

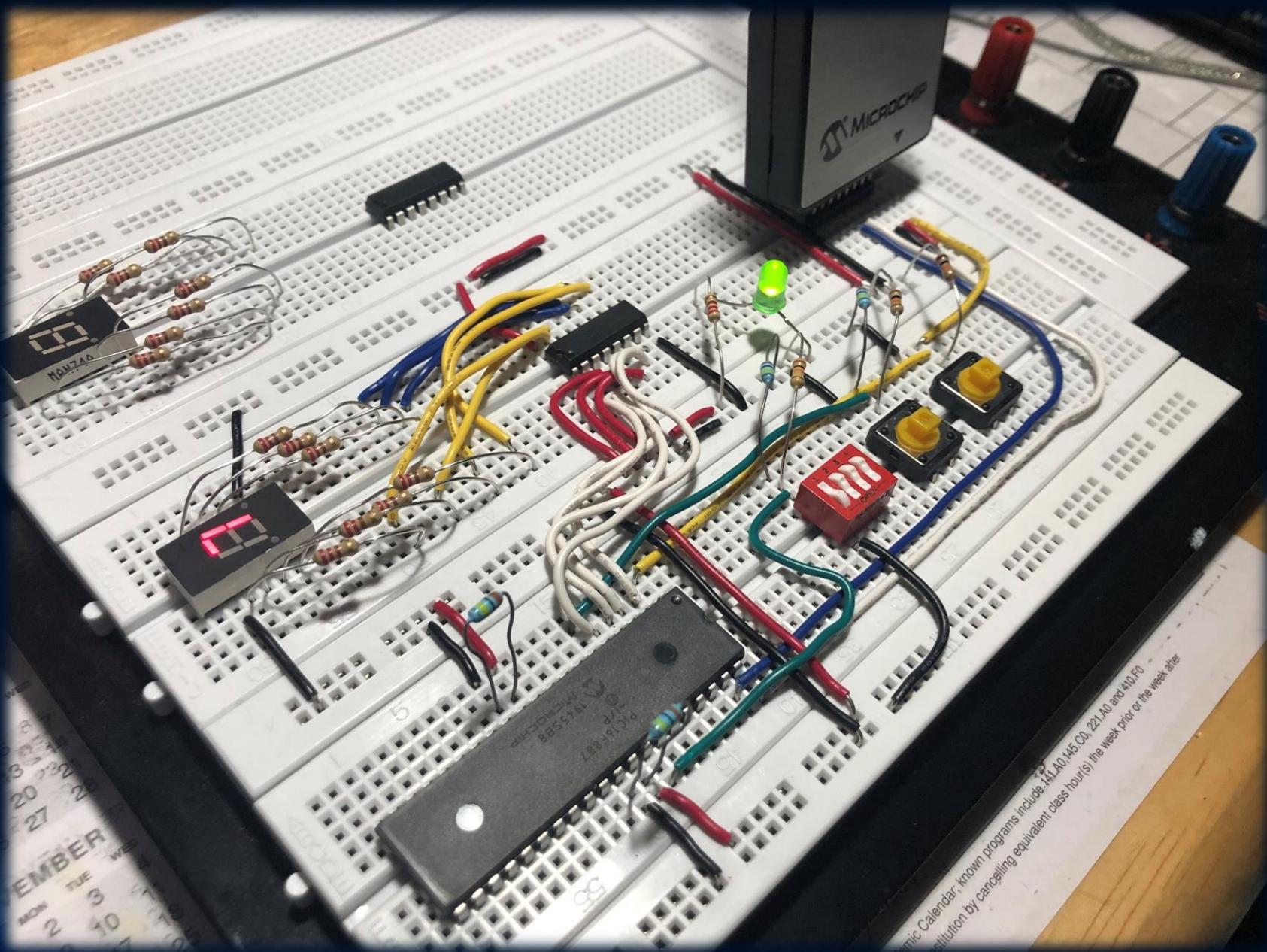

Final circuit prototype

The screenshot shows the MPLAB X IDE interface. The top menu bar includes Edit, View, Navigate, Source, Refactor, Production, Debug, Team, Tools, Window, Help, and a search bar. The main window has several tabs: Projects, PartA.asm, PartB.asm, and PartC.asm. The Projects tab shows a tree view of the LabAssignment project with subfolders like Header Files, Important Files, Linker Files, Source Files, and Libraries. The PartA.asm tab displays assembly code:

```
33      org      0x0000 ; Address of the first program instruction.
34      goto    Main      ; Go to "Main".
35
36      ;*****
37      ;[Interrupt routine]
38
39      ;GIE bit in INTCON is cleared upon entering this interrupt routine.
40
41      org      0x0004 ; Interrupt vector.
42
43      movwf   W_TEMP ; Move Wreg to W_TEMP register.
44      swapf   STATUS,w ; Swap STATUS register to be placed in Wreg.
45      movwf   STATUS_TEMP ; Move STATUS (in Wreg) to STATUS_TEMP register.
46
47      ;for UP-counter:
48      btiss   PORTB,RB0 ; If RB0 reads 0 (LOW), next instruction will be executed, otherwise SKIPPED.
49      inef    PORTA,f ; Increments counter (PORTA) by 1, then result is stored in PORTA register.
50      btiss   PORTB,RB0 ; If RB0 reads 0 (LOW), next instruction will be executed, otherwise SKIPPED.
51      call    UP_CHECK ; Call UP_CHECK subroutine (below).
```

The PartB.asm tab is currently active. The PartC.asm tab shows a memory usage summary:

Memory Type	Used	Free
Data 368 (0x170) bytes	0%	Data Used: 0 (0x0) Free: 368 (0x170)
Program 8,192 (0x2000) words	1%	Program Used: 78 (0x4E) Free: 8,114 (0x1FB2)

The Output tab shows the simulator launching and stopping at a breakpoint:

```
Launching
Initializing simulator
User program running
Breakpoint hit at line 44 in file C:/Users/Leonardo Fussner/Documents/MPLAB X projects/Micro/LabAssignment/PartC.asm.
User program stopped
```

The Watches tab displays register values:


Name	Type	Address	Value
WREG	NMMR	0x0	0x00
TMR0	SFR	0x1	0x00
STATUS	SFR	0x3	0x1C
PORTA	SFR	0x5	0x00
PORTB	SFR	0x6	0x01
INTCON	SFR	0x8	0x26

Software Approach

LOGIC, FLOWCHART & IMPLEMENTATION


The Logic

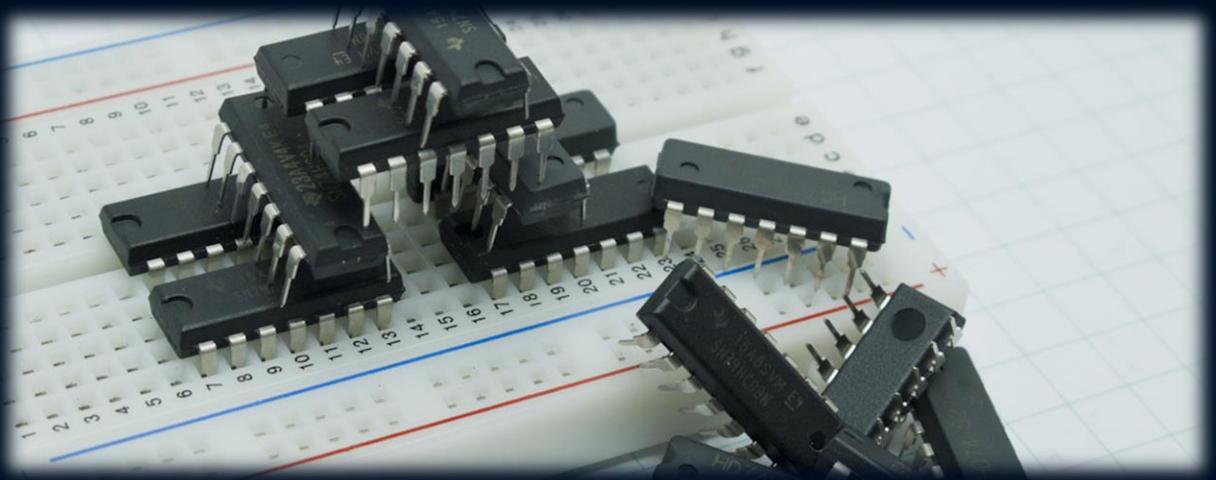- For UP-counter -> *o to 9*
- For DOWN-counter -> *9 to o*
- Implement condition control for UP/DOWN-counter
- Implement condition evaluation in Assembly language (for threshold check)
- Use interrupts for UP/DOWN-count functionality.
- Keep **1-second delay** for UP/DOWN-counter!





Flowchart

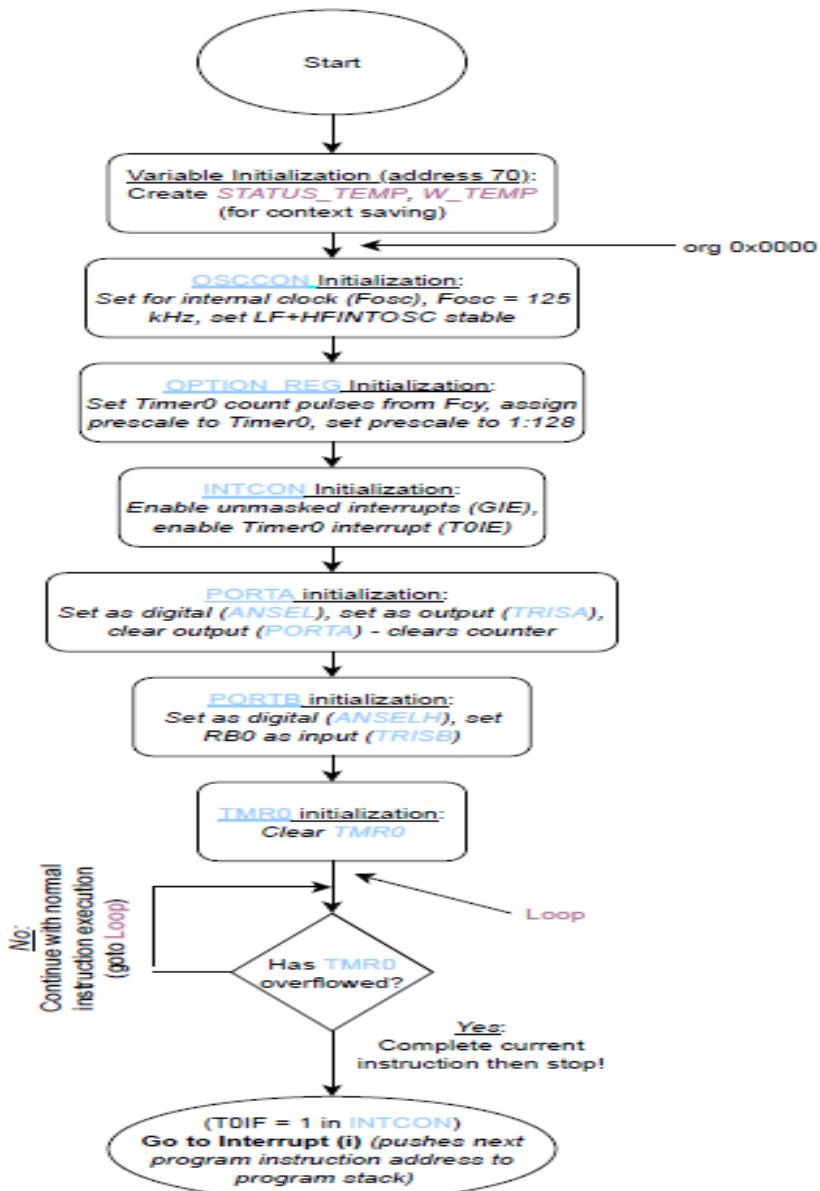Microcontroller & Microprocessor systems
Day Yann Fong
Lab Assignment - Part C Flowchart (I)



Leonardo Fusser (1946995)

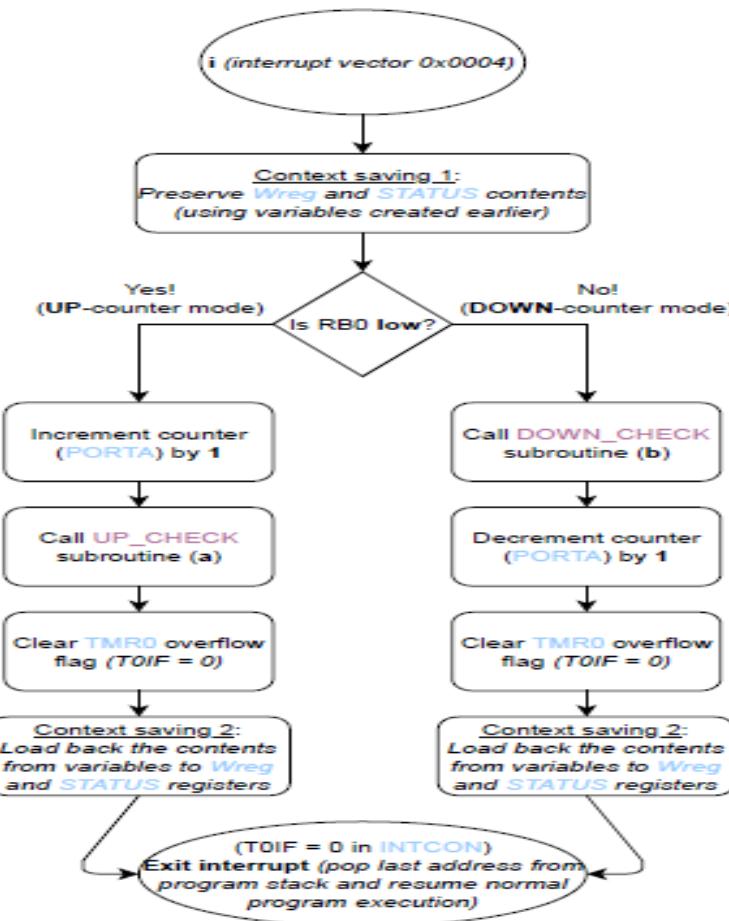

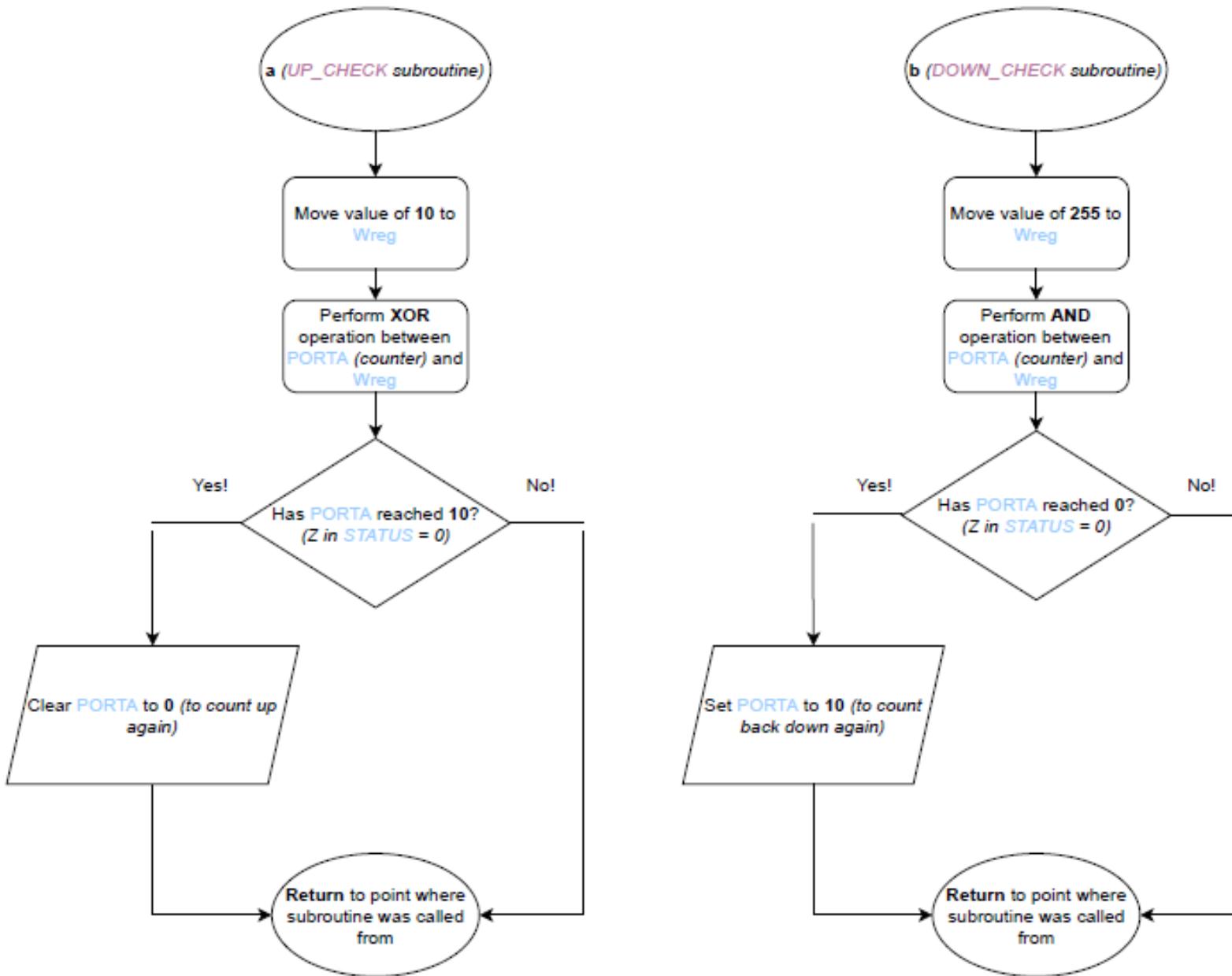

Implementation

- Must read pin status using bit-oriented file register operations (*BTFSS*, *BTFSC*)
- Must use byte-oriented file register operation for condition evaluation:
 - *Use XOR operation for UP-counter*
 - *Use AND operation for DOWN-counter*
- Check Z in **STATUS register** to determine if condition yields true!

XOR Truth Table

Inputs		Output
A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

*Same logic used for UP-counter
conditional check*

AND Truth Table

Inputs		Output
A	B	$Y = A.B$
0	0	0
0	1	0
1	0	0
1	1	1

*Same logic used for DOWN-counter
conditional check*

PIC16F882/883/884/886/887

TABLE 15-2: PIC16F882/883/884/886/887 INSTRUCTION SET

Mnemonic, Operands	Description	Cycles	14-Bit Opcode		Status Affected	Notes
			MSb	LSb		
BYTE-ORIENTED FILE REGISTER OPERATIONS						
ADDWF	f, d	Add W and f	1	00 0111 dfff ffff	C, DC, Z	1, 2
ANDWF	f, d	AND W with f	1	00 0101 dfff ffff	Z	1, 2
CLRF	f	Clear f	1	00 0001 1fff ffff	Z	2
CLRW	-	Clear W	1	00 0001 0xxx xxxx	Z	
COMF	f, d	Complement f	1	00 1001 dfff ffff	Z	1, 2
DECFSZ	f, d	Decrement f, Skip if 0	1(2)	00 1011 dfff ffff	Z	1, 2, 3
INCF	f, d	Increment f	1	00 1010 dfff ffff	Z	1, 2
INCFSZ	f, d	Increment f, Skip if 0	1(2)	00 1111 dfff ffff	Z	1, 2, 3
IORWF	f, d	Inclusive OR W with f	1	00 0100 dfff ffff	Z	1, 2
MOVF	f, d	Move f	1	00 1000 dfff ffff	Z	1, 2
MOVWF	f	Move W to f	1	00 0000 1fff ffff	Z	
NOP	-	No Operation	1	00 0000 0xx0 0000		
RLF	f, d	Rotate Left f through Carry	1	00 1101 dfff ffff	C	1, 2
RRF	f, d	Rotate Right f through Carry	1	00 1100 dfff ffff	C	1, 2
SUBWF	f, d	Subtract W from f	1	00 0010 dfff ffff	C, DC, Z	1, 2
SWAPF	f, d	Swap nibbles in f	1	00 1110 dfff ffff	Z	1, 2
XORWF	f, d	Exclusive OR W with f	1	00 0110 dfff ffff	Z	1, 2

Excerpt taken from pg. 227 of PIC 16F887 datasheet

PIC16F882/883/884/886/887

TABLE 15-2: PIC16F882/883/884/886/887 INSTRUCTION SET

Mnemonic, Operands	Description	Cycles	14-Bit Opcode		Status Affected	Notes
			MSb	LSb		
BYTE-ORIENTED FILE REGISTER OPERATIONS						
ADDWF f, d	Add W and f	1	00 0111	dfff ffff	C, DC, Z	1, 2
ANDWF f, d	AND W with f	1	00 0101	dfff ffff	Z	1, 2
CLRF f	Clear f	1	00 0001	1fff ffff	Z	2
CLRW -	Clear W	1	00 0001	0xxx xxxx	Z	
COMF f, d	Complement f	1	00 1001	dfff ffff	Z	1, 2
DECFSZ f, d	Decrement f, Skip if 0	1(2)	00 0011	dfff ffff	Z	1, 2
INCF f, d	Increment f	1	00 1010	dfff ffff	Z	1, 2
INCFSZ f, d	Increment f, Skip if 0	1(2)	00 1111	dfff ffff	Z	1, 2, 3
IORWF f, d	Inclusive OR W with f	1	00 0100	dfff ffff	Z	1, 2
MOVF f, d	Move f	1	00 1000	dfff ffff	Z	1, 2
MOVWF f	Move W to f	1	00 0000	1fff ffff		
NOP -	No Operation	1	00 0000	0xx0 0000		
RLF f, d	Rotate Left f through Carry	1	00 1101	dfff ffff	C	1, 2
RRF f, d	Rotate Right f through Carry	1	00 1100	dfff ffff	C	1, 2
SUBWF f, d	Subtract W from f	1	00 0010	dfff ffff	C, DC, Z	1, 2
SWAPF f, d	Swap nibbles in f	1	00 1110	dfff ffff		1, 2
XORWF f, d	Exclusive OR W with f	1	00 0110	dfff ffff	Z	1, 2

Excerpt taken from pg. 227 of PIC 16F887 datasheet

```
;for UP-counter:  
btfs  PORTB,RB0 ; If RB0 reads 0 (LOW), next instruction will be executed, otherwise SKIPPED.  
incf  PORTA,f ; Increments counter (PORTA) by 1, then result is stored in PORTA register.  
btfs  PORTB,RB0 ; If RB0 reads 0 (LOW), next instruction will be executed, otherwise SKIPPED.  
call  UP_CHECK ; Call UP_CHECK subroutine (below).  
  
;for DOWN-counter:  
btfsc PORTB,RB0 ; If RB0 reads 1 (HIGH), next instruction will be executed, otherwise SKIPPED.  
call  DOWN_CHECK ; Call subroutine DOWN_CHECK (below).  
btfsc PORTB,RB0 ; If RB0 reads 1 (HIGH), next instruction will be executed, otherwise SKIPPED.  
decf  PORTA,f ; Decrements counter (PORTA) by 1, then result is stored in PORTA register.
```

Implementation done in ISR and through subroutines

```
;Subroutine for checking if counter (PORTA) has reached 10.
```

```
UP_CHECK
```

```
    movlw    b'00001010'      ; 10 in binary (in Wreg).
    xorwf    PORTA,w         ; Performs XOR operation between Wreg (value of 10) and value stored in PORTA (value of counter).
    btfsc    STATUS,Z         ; Checks to see if zero flag is set (from XOR operation above), otherwise next instruction is SKIPPED.
    clrf    PORTA             ; Clears counter back down to zero if the previous instruction yields TRUE.
    clrw
    return                         ; Return to point where subroutine was called from.
```

Subroutine to check if UP-counter reached threshold

```
;Subroutine for checking if counter (PORTA) has reached 255.
```

```
DOWN_CHECK
```

```
    movlw    b'11111111'      ; 255 in binary.
    andwf    PORTA,w         ; Performs AND operation between Wreg (value of 255) and value stored in PORTA (value of counter).
    btfsc    STATUS,Z         ; Checks to see if zero flag is set (from AND operation above), otherwise next instruction is SKIPPED.
    movlw    b'00001010'      ; 10 in binary (in Wreg).
    btfsc    STATUS,Z         ; Checks to see if zero flag is set (from AND operation above), otherwise next instruction is SKIPPED.
    movwf    PORTA             ; Moves value of 10 (in Wreg) to counter if previous instruction yields TRUE.
    clrw
    return                         ; Return to point where subroutine was called from.
```

Subroutine to check if DOWN-counter reached threshold

Observation table for 4-bit binary UP counter (0 – 9)

Decimal value	(Value of 00001010 is moved to Wreg when subroutine is called)		Z flag in STATUS	PORTA goes back to 0?
	Value of counter (PORTA)	Result after xorwf PORTA,w		
0	00000000	00001010	0	No
1	00000001	00001011	0	No
2	00000010	00001000	0	No
3	00000011	00001001	0	No
4	00000100	00001110	0	No
5	00000101	00001111	0	No
6	00000110	00001100	0	No
7	00000111	00001101	0	No
8	00001000	00000010	0	No
-> 9	00001001	00000011	0	No
10**	00001010	00000000	1	Yes!

*Note: for Z flag in STATUS register, 0 -> not set (no zero) & 1 -> is set (is zero)!

**Although not shown on 7-segment, it does count up to 10 in background.

Observation done through MPLAB X IDE simulator/debugger

Observation table for 4-bit binary DOWN counter (9 - 0)

Decimal value	(Value of 11111111 is moved to Wreg when subroutine is called)		Z flag in STATUS	PORTA goes back to 9?
	Value of counter (PORTA)	Result after andwf PORTA,w		
10**	00001010	00001010	0	No
-> 9	00001001	00001001	0	No
8	00001000	00001000	0	No
7	00000111	00000111	0	No
6	00000110	00000110	0	No
5	00000101	00000101	0	No
4	00000100	00000100	0	No
3	00000011	00000011	0	No
2	00000010	00000010	0	No
1	00000001	00000001	0	No
0	00000000	00000000	1	Yes!


*Note: for Z flag in STATUS register, 0 -> not set (no zero) & 1 -> is set (is zero)!

**Although not shown on 7-segment, it does count down from 10 in background.

Observation done through MPLAB X IDE simulator/debugger

```
Entity FFmux is
port( rst, clk, ctrl, a, b: in bit;
      q: out bit);
end FFmux;

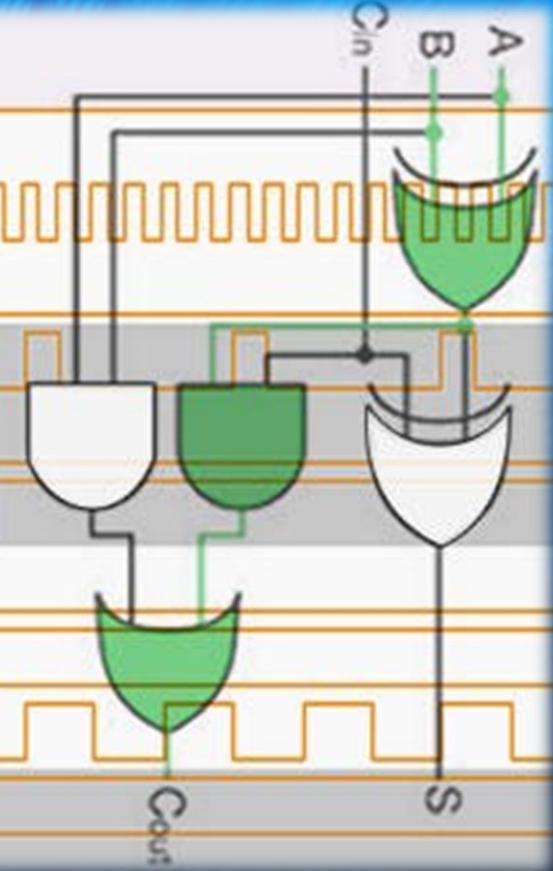architecture Func of FFmux is
begin
  process (rst, clk)
  begin
    if rst = '1' then
      q <= '0';
    elsif clk'event and clk = '1' then
      if ctrl = '1' then q <= a;
        else q <= b;
      end if;
    end if;
  end process;
end Func;
```




Problems Encountered & Solutions

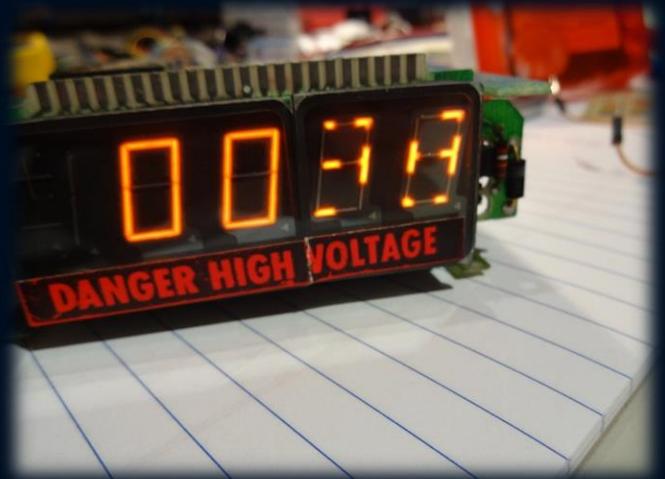PROBLEMS & MPLAB X IDE SIMULATOR

The Problem

- For UP-counter -> $0 - 8$ instead of $0 - 9$
- For DOWN-counter -> $8 - 0$ instead of $9 - 0$
- Solution: debugging with MPLAB X IDE simulator!




Screenshot of the MPLAB X IDE Watches window:

Name	Type	Address	Value
WREG	NMMR	...	0x00
TMR0	SFR	0x1	0x02
STATUS	SFR	0x3	0x3C
PORTA	SFR	0x5	0x00
PORTB	SFR	0x6	0x01
INTCON	SFR	0xB	0xA2


Below the table, there is a placeholder row: <Enter new watch>

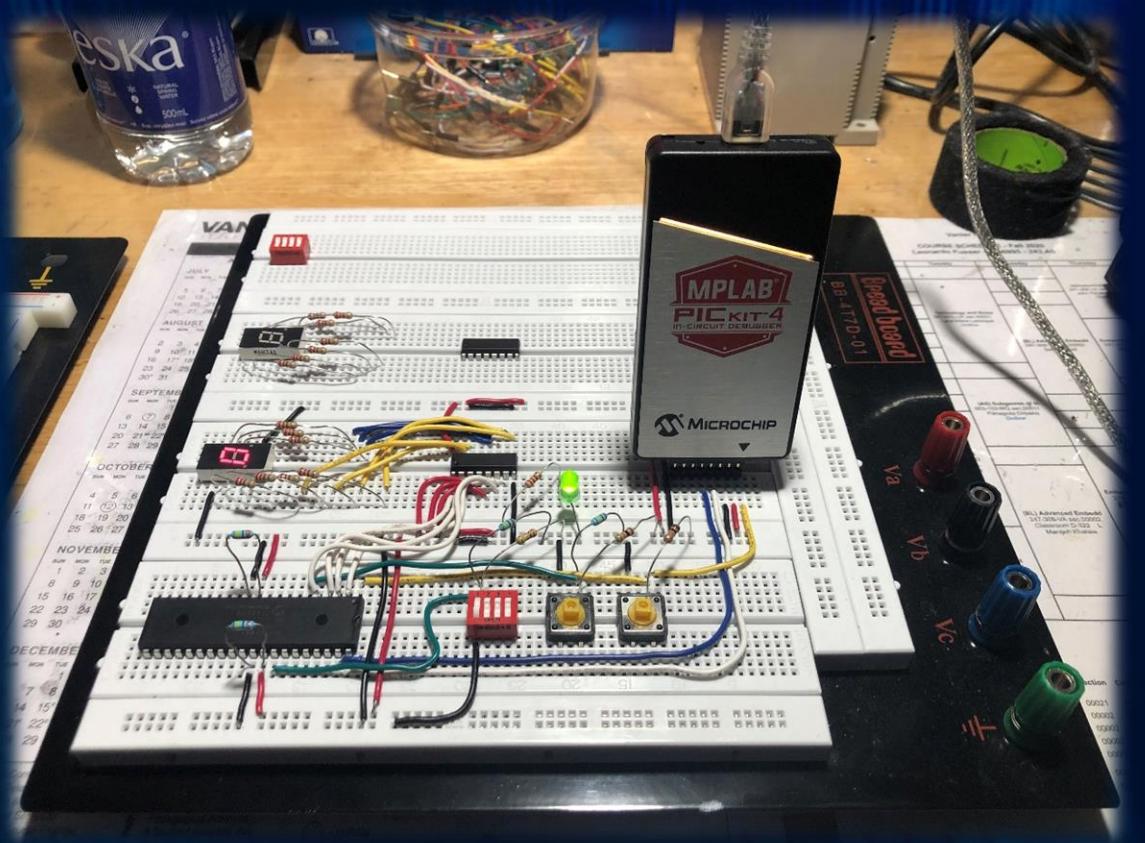At the bottom of the window, there are tabs for 'LabAssignment (Build, Load, ...)', 'debugger halted', and status indicators for memory usage (2), assembly address (131:1), and assembly language (INS).



```
entity FFmux is
port( rst, clk, ctrl, a, b: in bit;
      q: out bit);
end FFmux;

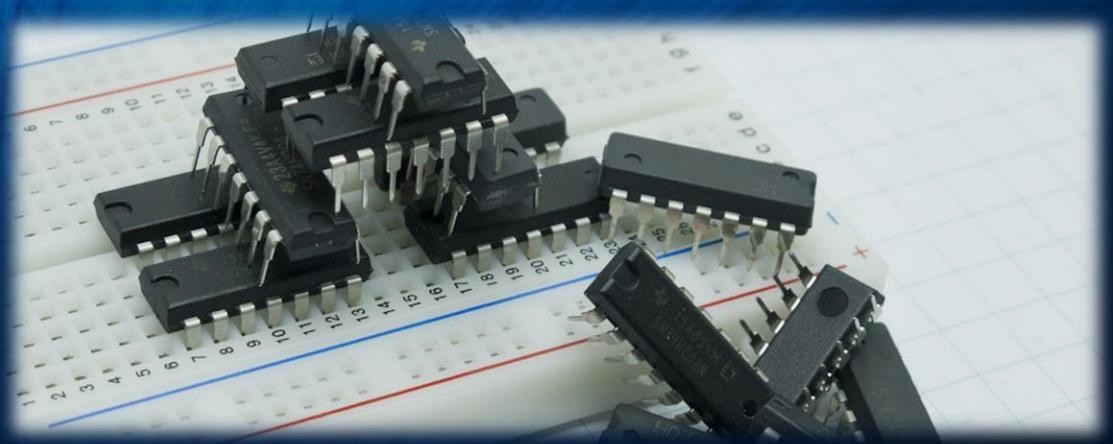architecture Func of FFmux is
begin
process (rst, clk)
begin
  if rst = '1' then
    q <= '0';
  elsif clk event and clk = '1' then
    if ctrl = '1' then q <= a;
    else q <= b;
  end if;
end if;
end process;
end Func;
```



Take away from this assignment

LESSONS LEARNED & WHAT I CAN IMPROVE ON...

Take away...

- *Learned* how to use a 7-segment display
- *Learned* how to use a 7448 decoder/7-segment display driver
- *Learned* how to implement the display with PIC 16F887
- *Learned* how to implement conditional statement in Assembly
- To improve: be more comfortable with the simulator/debugger!