

# **Computer Circuit Fundamentals (Lab 7)**

*K-Maps*

**Leonardo Fusser, 1946995**

Experiment Performed on **1 November 2019**  
Report Submitted on **8 November 2019**

Department of Computer Engineering Technology  
*Computer Circuit Fundamentals*  
*Subash Handa*

## **TABLE OF CONTENTS**

Objectives .....	3
Design .....	3
Schematics.....	3
Questions.....	4

## OBJECTIVES

- Practice simplifying Boolean expressions.
- Practice using K-maps.
- Practice designing Logic circuits effectively.
- Practice simplifying Boolean expressions using K-maps.


## DESIGN

### Experiment


- This experiment consisted of simplifying a Boolean expression derived from a truth table using the K-map method. The simplified expression:  $AB' + CD'$ , was then implemented into two separate Logic circuits. The first Logic circuit, using the Boolean expression simplified before, was implemented using only NAND gates (7400 ICs). The second Logic circuit, using the same expression as before, was implemented using only NOR gates (7402 ICs).

## SCHEMATICS
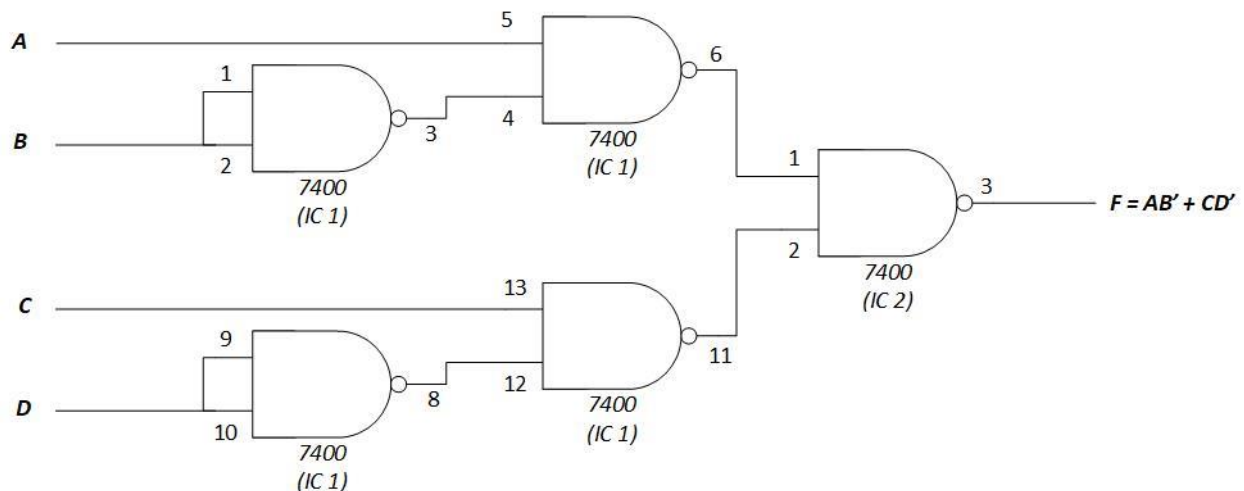
### $F = AB' + CD'$ (Logic Diagram using NANDs)



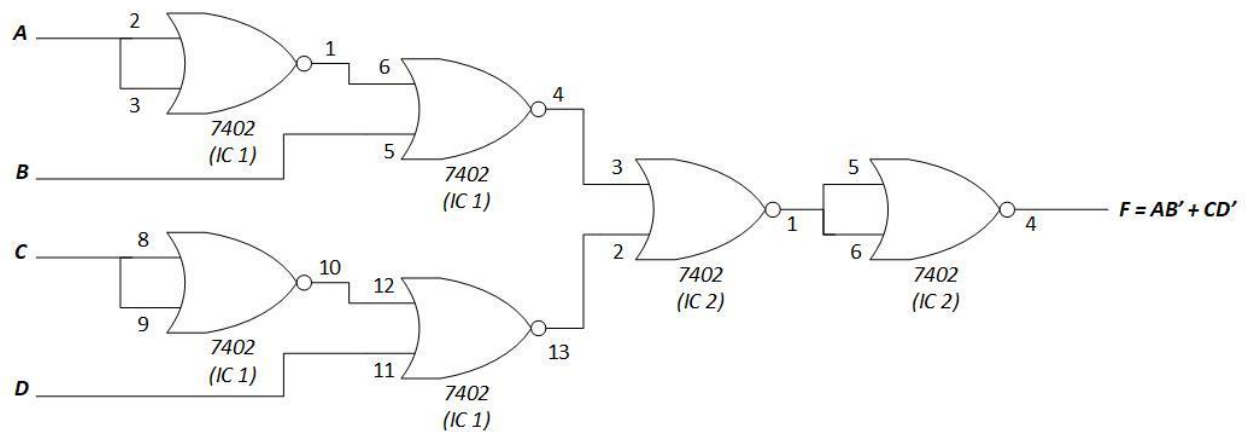**$F = AB' + CD'$  (Logic Diagram using NORs)**



## QUESTIONS

### Questions from the Experiment

INPUTS				OUTPUT
A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

**1) Simplification of the above truth table using K-maps:**

00	01	11	10
0	0	0	1
0	0	0	1
0	0	0	1
1	1	1	1

**2) Logical circuits**

- \* The drawn logic diagram could be found above, under "Schematics".*
- \* The logic diagram was shown to the instructor.*

**3) Verification**

- \* The Logic circuit was tested during the lab session.*
- \* The Logic circuit was verified using the truth table above.*