

# **Voltage Dividers and Potentiometers (Lab 8)**

*Experimenting with Voltage Dividers and Pots*

**Leonardo Fusser, 1946995**

Experiment Performed on **21 October 2019**  
Report Submitted on **28 October 2019**

**Department of Computer Engineering Technology**  
*Circuit Analysis & Simulation I*  
**Mohamed Tavakoli**

**VANIER**  
C É G E P / C O L L E G E  
Learning today Leading tomorrow

## **TABLE OF CONTENTS**

1.0 Purpose.....	3
2.0 Equipment Needed.....	3
3.0 Theory.....	3
4.0 Experiemntal Results .....	4
5.0 Conclusion .....	7

## 1.0 PURPOSE

- Understand the concept of the *Voltage Divider Rule*.
- Calculating voltage of resistors using *Voltage Divider Rule*.
- Measuring resistance of various positions on a Potentiometer.
- Understanding the concept of the Potentiometer.

## 2.0 EQUIPMENT NEEDED

- (1x) desktop Power Supply.
- (1x) desktop Digital Multimeter.
- (2x) 4-band (1/4 watt) resistors.
- (1x) Potentiometer.
- (1x) electronics breadboard.


## 3.0 THEORY

### *Voltage Divider*

- A **VOLTAGE DIVIDER** is a passive linear circuit that produces an output voltage that is a fraction of its input voltage. Voltage division is the result of distributing the input voltage among the components of the divider. (refer to Fig.1.).

(Document #1 – Voltage Divider Circuit)

**Fig.1.**

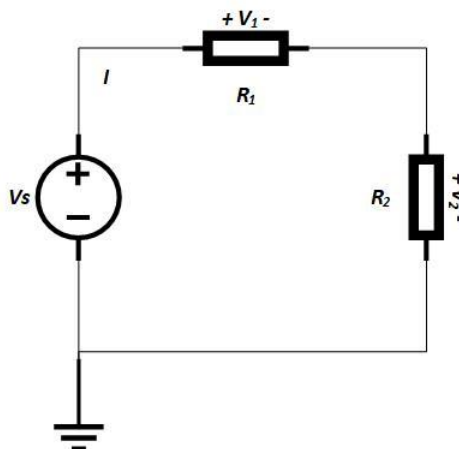

[To find  $V_0$ :]

$$R_T = R_1 + R_2$$

$$I = \frac{V_S}{R_T}$$

[Applying Ohm's law:]

$$V_1 = IR_1 = \left(\frac{V_S}{R_T}\right)R_1 = \frac{R_1 V_S}{R_T}$$

$$V_0 = IR_2 = \left(\frac{V_S}{R_T}\right)R_2 = \frac{R_2 V_S}{R_T}$$


[We can conclude from the above that:]

$$V_X = \frac{R_X V_S}{R_T} \text{ (Voltage Divider Rule)}$$

### Potentiometers (Pots)

- A **POTENTIOMETER** is a three-terminal resistor with a sliding or rotating contact that forms an adjustable voltage divider. If only two terminals are used, one end and the wiper, it acts as a variable resistor or rheostat (refer to Document #1 for reference).

(Document #1-Potentiometer)

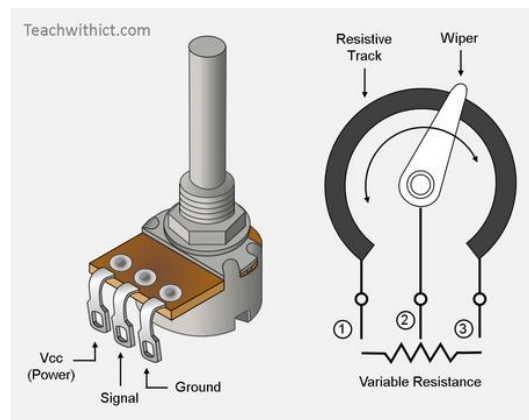

## 4.0 EXPERIMENTAL RESULTS

*Results from the Procedure section:*

### VOLTAGE DIVIDER:

**PROCEDURE:** ( $V_S = 12V$ ) (Use Circuit Fig.1 from above)

Step 1: Measure the values of the resistors and copy to Table 1.

**Step 2: Calculate the voltages of each resistor using the *Voltage Divider Rule* and copy to Table 1.**

**Step 3: Calculate the current in each resistor and write in Table 1.**

**Step 4: Build the circuit of Fig.1.**

**Step 5: Ask your teacher to verify your circuit before you connect power supply.**

**Step 6: Set the voltage source to 12V and limit the current to 500mA.**

**Step 7: Measure the voltages of each resistor and copy to Table 1.**

**Step 8: Measure the current of each resistor and copy to Table 1.**

**Step 9: Verify that Voltage Divider Rule is valid.**

<b>R<sub>T</sub> = 4.3KΩ</b>		<b>Voltage</b>			<b>Current</b>		
<b>Resistor</b>	<b>Value</b>	<b>Calculated</b>	<b>Measured</b>	<b>%Error</b>	<b>Calculated</b>	<b>Measured</b>	<b>%Error</b>
<b>R1</b>	1KΩ	2.79V	3.0V	7.5%	2.79mA	2.5mA	10.3%
<b>R2</b>	3.3KΩ	9.20V	8.8V	4.3%	2.79mA	2.5mA	10.3%

**CALCULATIONS:**

[Calculated Voltage]

$$V_x = \frac{R_x * V_S}{R_T}, = \frac{1K\Omega * 12V}{4.3K\Omega} = \mathbf{2.79V}$$

$$V_x = \frac{R_x * V_S}{R_T}, = \frac{3.3K\Omega * 12V}{4.3K\Omega} = \mathbf{9.20V}$$

[%Error Voltage]

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{3.0V - 2.79V}{2.79V} * 100 = \mathbf{7.5\%}$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{8.8V - 9.20V}{9.20V} * 100 = \mathbf{4.3\%}$$

[Calculated Current]

$$V = I * R, 2.79 = I * 1K\Omega, I = \mathbf{2.79mA}$$

$$V = I * R, 9.20 = I * 3.3K\Omega, I = \mathbf{2.79mA}$$


[%Error Current]

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{2.5mA - 2.79mA}{2.79mA} * 100 = \mathbf{10.3\%}$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{2.5mA - 2.79mA}{2.79mA} * 100 = \mathbf{10.3\%}$$

**POTENTIOMETER:**

**Fig.2.**

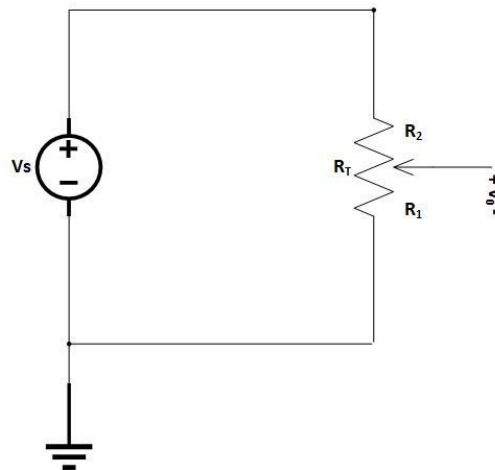

**PROCEDURE:** ( $V_S = 12V$ ) (Use Circuit Fig.2.)

- Step 1: Measure the value of the total resistance (Fixed resistance) and copy it to table 2.
- Step 2: Divide the fixed resistance in four parts (25%, 50%, 75% and 100%) and calculate the voltages for each part using the *Voltage Divider Rule* to copy to Table 2.
- Step 3: Calculate the current in each resistor and write in Table 2.
- Step 4: Build the circuit of Fig.2.
- Step 5: Ask your teacher to verify your circuit before you connect power supply.
- Step 6: Set the voltage source to 12V and limit the current to 500mA.
- Step 7: Set the wiper arm to the 4 parts (approximate) and measure the voltages  $V_0$  for each setting and copy to table 2.
- Step 8: Measure the current of each resistor and copy to Table 2.
- Step 9: You might have a non-linear pot, make a note of that!

Fixed = 7.2K $\Omega$		Voltage			Current		
Resistor	Value	Calculated	Measured	%Error	Calculated	Measured	%Error
25%	1.75K $\Omega$	2.9V	2.7V	6.8%	1.65mA	1.4mA	15.6%
50%	2.8K $\Omega$	4.6V	4.4V	4.3%	1.64mA	1.4mA	14.6%
75%	5K $\Omega$	8.3V	8.1V	2.4%	1.66mA	1.4mA	15.6%
100%	7.2K $\Omega$	12V	11.9V	0.08%	1.67mA	1.4mA	16.1%

**CALCULATIONS:**

[Calculated Voltage]

$$V_X = \frac{R_X * V_S}{R_T}, = \frac{1.75K\Omega * 12V}{7.2K\Omega} = \mathbf{2.9V}$$

$$V_x = \frac{R_x * V_S}{R_T}, = \frac{2.8K\Omega * 12V}{7.2K\Omega} = 4.6V$$

$$V_x = \frac{R_x * V_S}{R_T}, = \frac{5K\Omega * 12V}{7.2K\Omega} = 8.3V$$

$$V_x = \frac{R_x * V_S}{R_T}, = \frac{7.2K\Omega * 12V}{7.2K\Omega} = 12V$$

[%Error Voltage]

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{2.7V - 2.9V}{2.9V} * 100 = 6.8\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{4.4V - 4.6V}{4.6V} * 100 = 4.3\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{8.1V - 8.3V}{8.3V} * 100 = 2.4\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{11.9V - 12V}{12V} * 100 = 0.08\%$$

[%Error Current]

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{1.4mA - 1.65mA}{1.65mA} * 100 = 15.6\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{1.4mA - 1.64mA}{1.64mA} * 100 = 14.6\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{1.4mA - 1.66mA}{1.66mA} * 100 = 15.6\%$$

$$\%Error = \frac{Measured - Calculated}{Calculated} * 100 = \frac{1.4mA - 1.67mA}{1.67mA} * 100 = 16.1\%$$

[Calculated Current]

$$V = I * R, 2.9 = I * 1.75K\Omega, I = 1.65mA$$

$$V = I * R, 4.6 = I * 2.8K\Omega, I = 1.64mA$$

$$V = I * R, 8.3 = I * 5K\Omega, I = 1.66mA$$

$$V = I * R, 12 = I * 7.2K\Omega, I = 1.67mA$$

## 5.0 CONCLUSION

- Understood the concept of the *Voltage Divider Rule*.
- Purpose of this lab has been achieved.
- Understood how to measure voltage of resistors using the *Voltage Divider Rule*.
- Understood how to measure resistance from various positions on a Potentiometer.
- Understood the concept of the Pots.
- Error occurred when measuring the voltage of a position in a Potentiometer: the probes were not connected correctly across the correct terminals.
- Solution: corrected the error from above and using the *Voltage Divider Formula* to double check that my measurements would read somewhat close to what was calculated.